
 


## 6. Combinational Circuits

 


George Boole (1815 - 1864)



Claude Shannon (1916 - 2001)

## Computer Architecture

TOY lectures. von Neumann machine.

 

This lecture. Boolean circuits.

Ahead. Putting it all together and building a TOY machine.

## Digital Circuits

### What is a digital system?

- Digital: signals are 0 or 1.
- Analog: signals vary continuously.

### Why digital systems?

- Accuracy and reliability.
- Staggeringly fast and cheap.

### Basic abstractions.

- On, off.
- Wire: propagates on/off value.
- Switch: controls propagation of on/off values through wires.


### Digital circuits and you.

- **Computer microprocessors.**
- Antilock brakes, cell phones, iPods, etc.

## Wires
 
### Wires.


- On (1): connected to power.
- Off (0): not connected to power.
- If a wire is connected to a wire that is on, that wire is also on.
- Typical drawing convention: "flow" from top, left to bottom, right.


 
## Controlled Switch


**Controlled switch.** [relay implementation]

- 3 connections: input, output, control.
- Magnetic force pulls on a contact that cuts electrical flow.
- Control wire affects output wire, but output does not affect control; establishes forward flow of information over time.



5

## Circuit Anatomy

 


6

## Layers of Abstraction

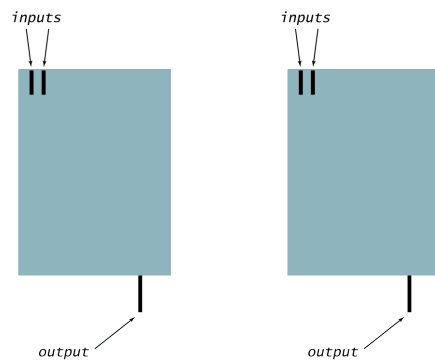**Layers of abstraction.**

- Circuits are built from wires and switches. (implementation)
- A circuit is defined by its inputs and outputs. (interface)
- To control complexity, we encapsulate circuits. (ADT)




7

## Layers of Abstraction

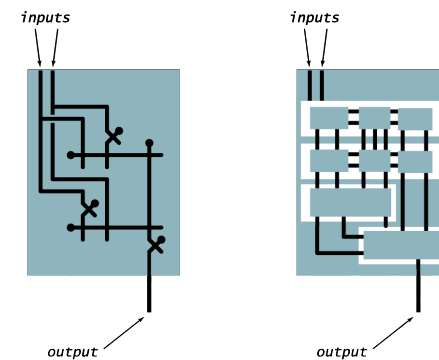**Layers of abstraction.**

- Circuits are built from wires and switches. (implementation)
- A circuit is defined by its inputs and outputs. (interface)
- To control complexity, we encapsulate circuits. (ADT)




8

## Logic Gates: Fundamental Building Blocks


**NOT =  $x'$**

x	NOT
0	1
1	0

 


**OR =  $x+y$**

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

 

**AND =  $xy$**

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

 


9

## Logic Gates: Fundamental Building Blocks


**NOT =  $x'$**

x	NOT
0	1
1	0

 


**OR =  $x+y$**

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

 

**AND =  $xy$**

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

 


implementations with switches

10

## Multiway Gates
 
### Multiway gates.

- OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.




11

## Multiway Gates

 
### Multiway gates.

- OR: 1 if any input is 1; 0 otherwise.
- AND: 1 if all inputs are 1; 0 otherwise.
- Generalized: negate some inputs.



12

## Cancelling inverters

 

13

## Boolean Algebra

### History.

- Developed by Boole to solve mathematical logic problems (1847).
- Shannon master's thesis applied it to digital circuits (1937).


"possibly the most important, and also the most famous, master's thesis of the [20th] century" --Howard Gardner

### Basics.

- Boolean variable: value is 0 or 1.
- Boolean function: function whose inputs and outputs are 0, 1.
 
### Relationship to circuits.

- Boolean variables: signals.
- Boolean functions: circuits.



14


## Truth Table

### Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs  $\Rightarrow 2^N$  rows.

x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

 

16

## Truth Table for Functions of 2 Variables

### Truth table.

- 16 Boolean functions of 2 variables.  $\leftarrow$  every 4-bit value represents one

x	y	ZERO	AND		x	y	XOR	OR
0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1
1	0	0	0	1	1	0	0	1
1	1	0	1	0	1	0	1	0

Truth table for all Boolean functions of 2 variables

x	y	NOR	EQ	y'		x'		NAND	ONE
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

Truth table for all Boolean functions of 2 variables

17

## Truth Table for Functions of 3 Variables

### Truth table.

- 16 Boolean functions of 2 variables. ← every 4-bit value represents one
- 256 Boolean functions of 3 variables. ← every 8-bit value represents one
- $2^{(2^n)}$  Boolean functions of n variables! ← every  $2^n$ -bit value represents one

x	y	z	AND	OR	MAJ	ODD
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1

Some Functions of 3 Variables

18

## Universality of AND, OR, NOT

**Fact.** Any Boolean function can be expressed using AND, OR, NOT.

- { AND, OR, NOT } are **universal**.
- Ex:  $XOR(x,y) = xy' + x'y$ .

Notation	Meaning
$x'$	NOT x
$xy$	x AND y
$x + y$	x OR y

### Expressing XOR Using AND, OR, NOT

x	y	$x'$	$y'$	$x'y$	$xy'$	$x'y + xy'$	x XOR y
0	0	1	1	0	0	0	0
0	1	1	0	1	0	1	1
1	0	0	1	0	1	1	1
1	1	0	0	0	0	0	0

**Exercise.** Show {AND, NOT}, {OR, NOT}, {NAND}, {AND, XOR} are universal.

**Hint.** DeMorgan's law:  $(x'y) = x + y$ .

19

## Sum-of-Products

**Sum-of-products.** Systematic procedure for representing a Boolean function using AND, OR, NOT.

- Form AND term for each 1 in Boolean function.
  - OR terms together.
- proves that { AND, OR, NOT } are universal

x	y	z	MAJ	$x'yz$	$xy'z$	$xyz'$	$xyz$	$x'yz + xy'z + xyz' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

expressing MAJ using sum-of-products

20

## Translate Boolean Formula to Boolean Circuit

**Sum-of-products.** XOR.

$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table



Circuit

21


### Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.


$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

 

Abstract circuit

 

Circuit


### Translate Boolean Formula to Boolean Circuit

Sum-of-products. XOR.


$$XOR = x'y + xy'$$

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

 

Abstract circuit

 

Circuit

### Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table



Circuit


### Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.


$$MAJ = x'yz + xy'z + xyz' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table

 

Abstract circuit

 


Circuit

## Translate Boolean Formula to Boolean Circuit

Sum-of-products. Majority.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

 


## Simplification Using Boolean Algebra

Many possible circuits for each Boolean function.

- Sum-of-products not necessarily optimal in:
  - number of switches (space)
  - depth of circuit (time)

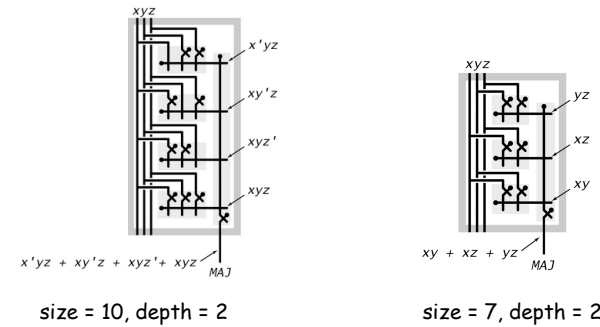Ex.  $MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz = xy + yz + xz.$



## Expressing a Boolean Function Using AND, OR, NOT

Ingredients.

- AND gates.
- OR gates.
- NOT gates.
- Wire.

Instructions.

- Step 1: represent input and output signals with Boolean variables.
- Step 2: construct truth table to carry out computation.
- Step 3: derive (simplified) Boolean expression using sum-of products.
- Step 4: transform Boolean expression into circuit.

## ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.

x	y	z	ODD	$x'y'z$	$x'yz'$	$xy'z'$	$xyz$	$x'y'z + x'yz' + xy'z' + xyz$
0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1
0	1	0	1	0	1	0	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	1	0	1
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	1	1

Expressing ODD using sum-of-products

## ODD Parity Circuit

ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.

$$MAJ = x'yz + xy'z + xyz' + xyz$$

$$ODD = x'y'z + x'yz' + xy'z' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



x	y	z	ODD
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



## ODD Parity Circuit


ODD(x, y, z).

- 1 if odd number of inputs are 1.
- 0 otherwise.


$$MAJ = x'yz + xy'z + xyz' + xyz$$

$$ODD = x'y'z + x'yz' + xy'z' + xyz$$

x	y	z	MAJ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

x	y	z	ODD
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

## Let's Make an Adder Circuit

Goal.  $x + y = z$  for 4-bit integers.


- We build 4-bit adder: 9 inputs, 4 outputs.
- Same idea scales to 128-bit adder.
- Key computer component.

Step 1. Represent input and output in binary.

1	1	1	0	
2	4	8	7	
+	3	5	7	9
<hr/>				
6	0	6	6	

1	1	0	0	
0	0	1	0	
+	0	1	1	1
<hr/>				
1	0	0	1	

	$x_3$	$x_2$	$x_1$	$x_0$
+	$y_3$	$y_2$	$y_1$	$y_0$
<hr/>				
	$z_3$	$z_2$	$z_1$	$z_0$

 

## Let's Make an Adder Circuit

Goal.  $x + y = z$  for 4-bit integers.

Step 2. (first attempt)

- Build truth table.
- Why is this a bad idea?
  - 128-bit adder:  $2^{256+1}$  rows > # electrons in universe!

$C_{out}$	$x_3$	$x_2$	$x_1$	$x_0$
+	$y_3$	$y_2$	$y_1$	$y_0$
	$z_3$	$z_2$	$z_1$	$z_0$

$C_0$	$x_3$	$x_2$	$x_1$	$x_0$	$y_3$	$y_2$	$y_1$	$y_0$	$z_3$	$z_2$	$z_1$	$z_0$
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	1	0	0	1	1	1
0	0	0	0	0	1	0	0	0	1	0	0	0
0	0	0	0	0	1	0	1	0	1	0	1	1
.	.	.	.	.	.	.	.	.	.	.	.	.
1	1	1	1	1	1	1	1	1	1	1	1	1

4-Bit Adder Truth Table

$2^{8+1} = 512$  rows!



### Let's Make an Adder Circuit

Goal.  $x + y = z$  for 4-bit integers.

Step 2. (do one bit at a time)

- Build truth table for carry bit.
- Build truth table for summand bit.

$c_{out}$	$c_3$	$c_2$	$c_1$	$c_0 = 0$
	$x_3$	$x_2$	$x_1$	$x_0$
+	$y_3$	$y_2$	$y_1$	$y_0$
	$z_3$	$z_2$	$z_1$	$z_0$

Carry Bit

$x_i$	$y_i$	$c_i$	$c_{i+1}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit

$x_i$	$y_i$	$c_i$	$z_i$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

### Let's Make an Adder Circuit

Goal.  $x + y = z$  for 4-bit integers.

Step 3.

- Derive (simplified) Boolean expression.

$c_{out}$	$c_3$	$c_2$	$c_1$	$c_0 = 0$
	$x_3$	$x_2$	$x_1$	$x_0$
+	$y_3$	$y_2$	$y_1$	$y_0$
	$z_3$	$z_2$	$z_1$	$z_0$

Carry Bit

$x_i$	$y_i$	$c_i$	$c_{i+1}$	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit


$x_i$	$y_i$	$c_i$	$z_i$	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### Let's Make an Adder Circuit


Goal.  $x + y = z$  for 4-bit integers.

Step 4.

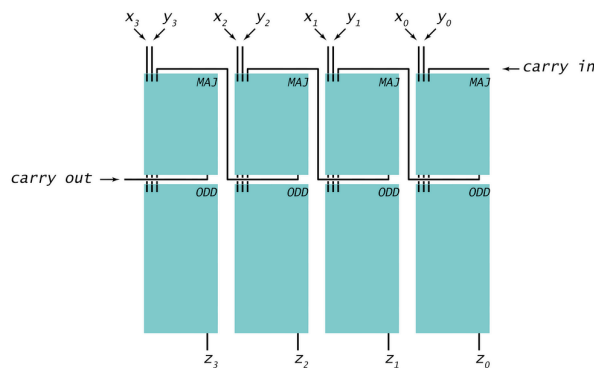
- Transform Boolean expression into circuit.
- Chain together 1-bit adders.





### Adder: Interface

 


Adder: Component Level View

 

Adder: Switch Level View

  

George Boole (1815 - 1864)

 

Claude Shannon (1916 - 2001)