

<https://introc.cs.princeton.edu>

7. DIGITAL CIRCUITS

- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *adder circuit*

Context

Q. How are computers built?


A. Not nearly as complicated as you might think.


This lecture. Introduction to **digital circuits**.

- Digital = all signals are either 0 or 1.
- Analog = signals vary continuously.
- Advantages of digital: accurate, reliable, fast, cheap, scalable, ...



 Applications. Laptop, smartphone, gaming console, pacemaker, microprocessor, ...



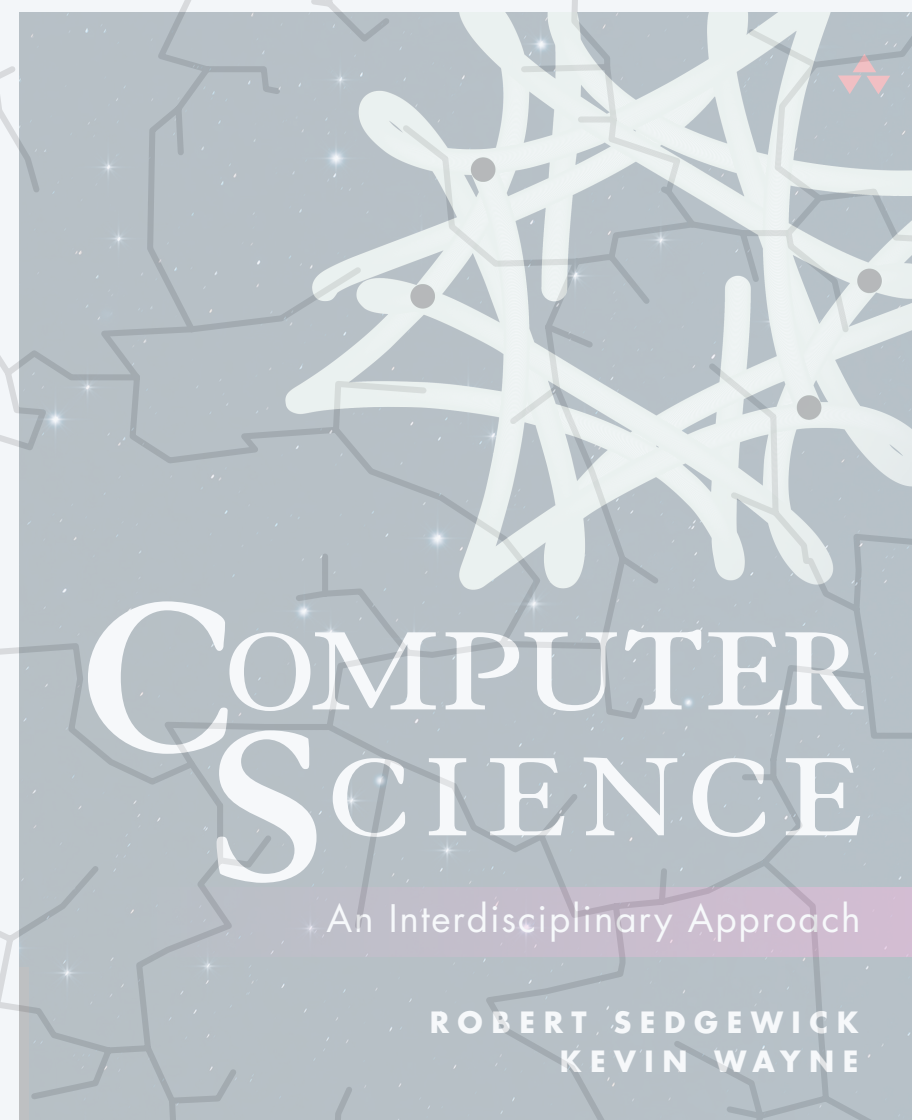

<https://introc.cs.princeton.edu>

7. DIGITAL CIRCUITS

- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *adder circuit*


Boolean algebra

Boolean algebra. Developed by George Boole in 1840s to study logic problems.

- Values of variables are *true* (1) or *false* (0).
- Primitive operations are *NOT*, *AND*, and *OR*.
- Widely used in mathematics, logic, computer science, ...

operation	logic notation	Java notation	circuit notation	precedence
<i>NOT</i>	$\neg x$	<code>!x</code>	x'	<i>highest</i>
<i>AND</i>	$x \wedge y$	<code>x && y</code>	$x \cdot y$	<i>middle</i>
<i>OR</i>	$x \vee y$	<code>x y</code>	$x + y$	<i>lowest</i>

↑
this lecture

 

George Boole is Coole



Copyright 2004, Sidney Harris

Relevance to circuits. Provides the mathematical foundation.

Truth tables

Boolean function. A function whose arguments and result assume the values 0 and 1.

Truth table. A systematic way to define a boolean function.

- One row for each possible assignment of arguments.
- Each row gives the function value for the specified arguments.
- The truth table of a boolean function of n variables has 2^n rows.

x	x'
0	1
1	0

NOT

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

AND

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR

x	y	z	$f(x, y, z)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

↑
count in binary from 0 to $2^n - 1$

Boolean algebra properties

Boolean algebra shares many properties with elementary algebra. ← *justifies use of \cdot and $+$ for AND and OR*

	property	AND	OR	
axioms	<i>commutative</i>	$x \cdot y = y \cdot x$	$x + y = y + x$	← <i>same as elementary algebra</i>
	<i>associative</i>	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) = (x + y) + z$	
	<i>identity</i>	$x \cdot 1 = x$	$x + 0 = x$	
	<i>distributive</i>	$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$	$x + (y \cdot z) = (x + y) \cdot (x + z)$	
	<i>complementary</i>	$x \cdot x' = 0$	$x + x' = 1$	
theorems	<i>idempotent</i>	$x \cdot x = x$	$x + x = x$	← <i>different from elementary algebra</i>
	<i>De Morgan</i>	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$	
	<i>duality</i>	<i>in any law, can interchange $+$ and \cdot, along with 0 and 1</i>		
	\vdots	\vdots	\vdots	

Proving a theorem in Boolean algebra

Q. How to prove a theorem, such as De Morgan's law?

A1. Apply sequence of axioms or known theorems.

A2. For each possible assignment of truth values to variables, evaluate the purported theorem; confirm that it is *true*.

← “method of perfect induction”

Ex. De Morgan's law: $(x \cdot y)' = (x' + y')$.

x	y	$x \cdot y$	$(x \cdot y)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

truth table for LHS

x	y	x'	y'	$x' + y'$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0


truth table for RHS

Boolean functions of two variables

Boolean function. A function whose arguments and result assume the values 0 and 1.

x	y	<i>AND</i>	<i>OR</i>	<i>NAND</i>	<i>NOR</i>	<i>XOR</i>
0	0	0	0	1	1	0
0	1	0	1	1	0	1
1	0	0	1	1	0	1
1	1	1	1	0	0	0

 commonly used boolean functions of 2 variables



Copyright 2010, Toothpaste for Dinner

Boolean functions of three (and more) variables

Boolean function. A function whose arguments and result assume the values 0 and 1.

<i>x</i>	<i>y</i>	<i>z</i>	<i>AND</i>	<i>OR</i>	<i>MAJ</i>	<i>ODD</i>
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	0	1	1	0
1	0	0	0	1	0	1
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	1	1

some boolean functions of 3 variables

function	shorthand	description
<i>logical AND</i>	<i>AND</i>	all inputs are 1
<i>logical OR</i>	<i>OR</i>	any input is 1
<i>majority</i>	<i>MAJ</i>	more inputs are 1 than 0
<i>odd parity</i>	<i>ODD</i>	odd number of inputs are 1

↑
*these functions all
extends to n variables*

Sum-of-products

Sum-of-products. Every boolean function can be represented as a sum of products.

- Products: form an *AND* term for each 1 in truth table.
- Sum: combine the terms with the *OR* function.

also known as
"disjunctive normal form"

x	y	z	MAJ	$x' \cdot y \cdot z$	$x \cdot y' \cdot z$	$x \cdot y \cdot z'$	$x \cdot y \cdot z$	
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	1	0	1
1	1	1	1	0	0	0	1	1

$(x' \cdot y \cdot z) + (x \cdot y' \cdot z) + (x \cdot y \cdot z') + (x \cdot y \cdot z) = MAJ$

Expressing MAJ(x, y, z) as a sum of products



Which of the following does NOT represent majority function?

A. $(x \cdot y) + (y \cdot z) + (x \cdot z)$

B. $z(x'y + xy') + xy$

C. $(x \cdot y) + (y \cdot z)$

D.

```
public static boolean majority(boolean x, boolean y, boolean z) {
    int count = 0;
    if (x) count++;
    if (y) count++;
    if (z) count++;
    return count >= 2;
}
```

Universality

Def. A set of operations is **universal** if every boolean function can be expressed using just those operations.

Proposition. $\{ AND, OR, NOT \}$ is a universal set of operations.


Pf. Sum-of-products construction on previous slide.


Proposition. $\{ NAND \}$ is a universal set of operations.

Pf. $\{ AND, OR, NOT \}$ can be constructed from $NAND$.

x	y	$NAND$
0	0	1
0	1	1
1	0	1
1	1	0

NAND

 

 

<https://introc.cs.princeton.edu>


7. DIGITAL CIRCUITS

- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *adder circuit*

A basis for digital devices

Claude Shannon. Identified the deep connection between **Boolean algebra** and **circuits**.

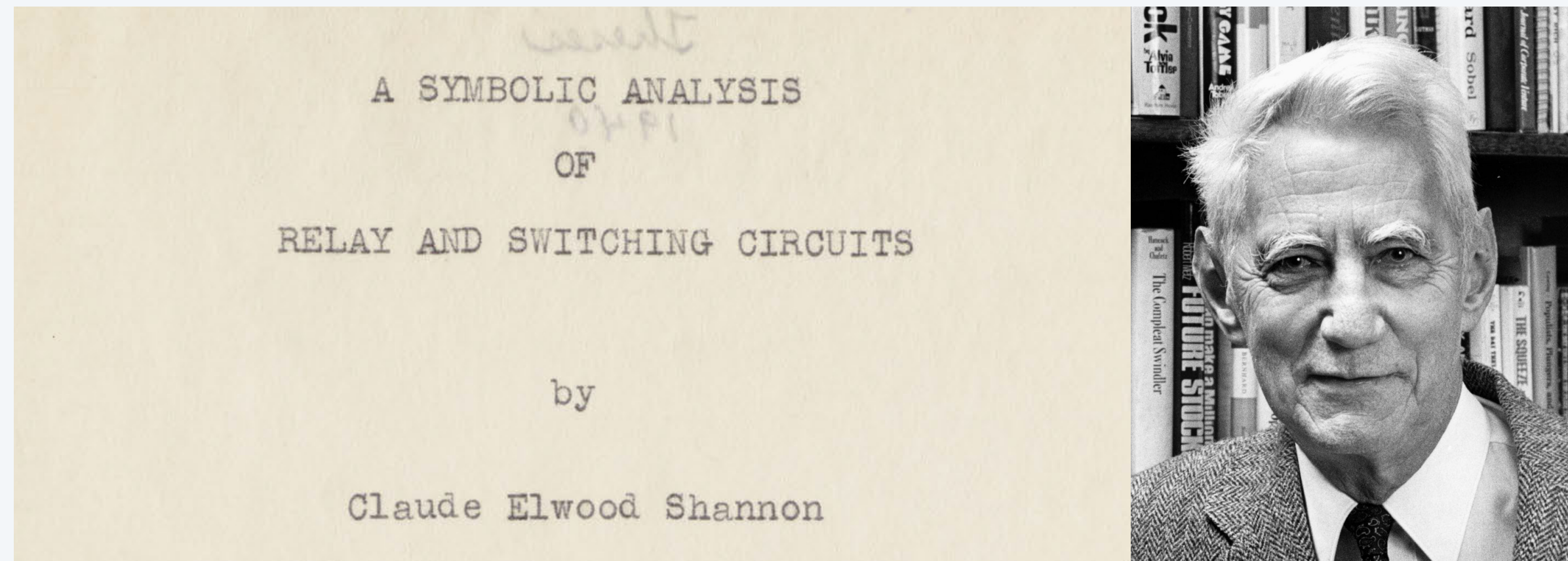- Demonstrated how circuits could be analyzed using Boolean algebra.
- Designed circuits to perform mathematical operations on binary numbers. ← *add, subtract, multiply, factor, ...*



Claude Shannon's master's thesis at MIT (1937)

Impact. Every electronic device we use today is based upon Shannon's foundational work.




The Bit Player



available on COS 126 Canvas
(movie features Dean Andrea Goldsmith)

Primitive logic gates: AND, OR, and NOT


Logic gate. Physical device that implement a boolean function with one output.

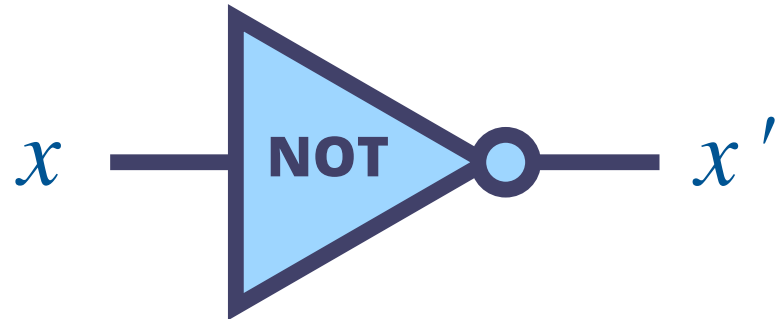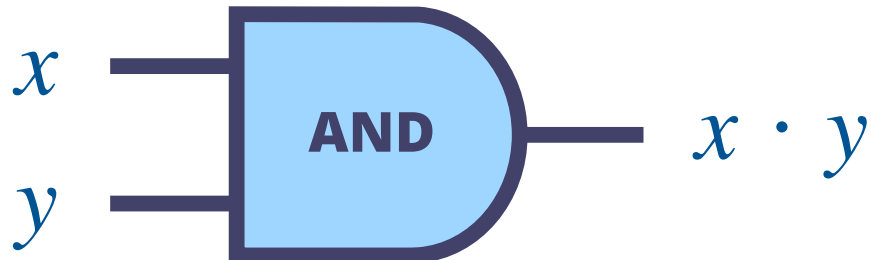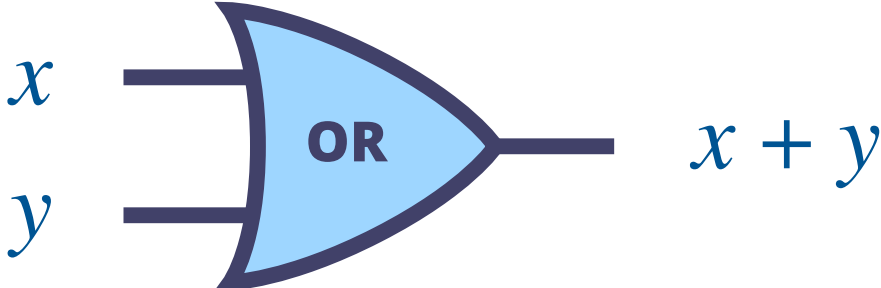gate	truth table	notation	symbol															
<i>NOT</i> (inverter)	<table border="1"> <thead> <tr> <th>x</th> <th><i>NOT</i></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	x	<i>NOT</i>	0	1	1	0	x'										
x	<i>NOT</i>																	
0	1																	
1	0																	
<i>AND</i>	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th><i>AND</i></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	x	y	<i>AND</i>	0	0	0	0	1	0	1	0	0	1	1	1	$x \cdot y$	
x	y	<i>AND</i>																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
<i>OR</i>	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th><i>OR</i></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	x	y	<i>OR</i>	0	0	0	0	1	1	1	0	1	1	1	1	$x + y$	
x	y	<i>OR</i>																
0	0	0																
0	1	1																
1	0	1																
1	1	1																

Digital circuits

Digital circuit. A network of **logic gates** connected by **wires**.

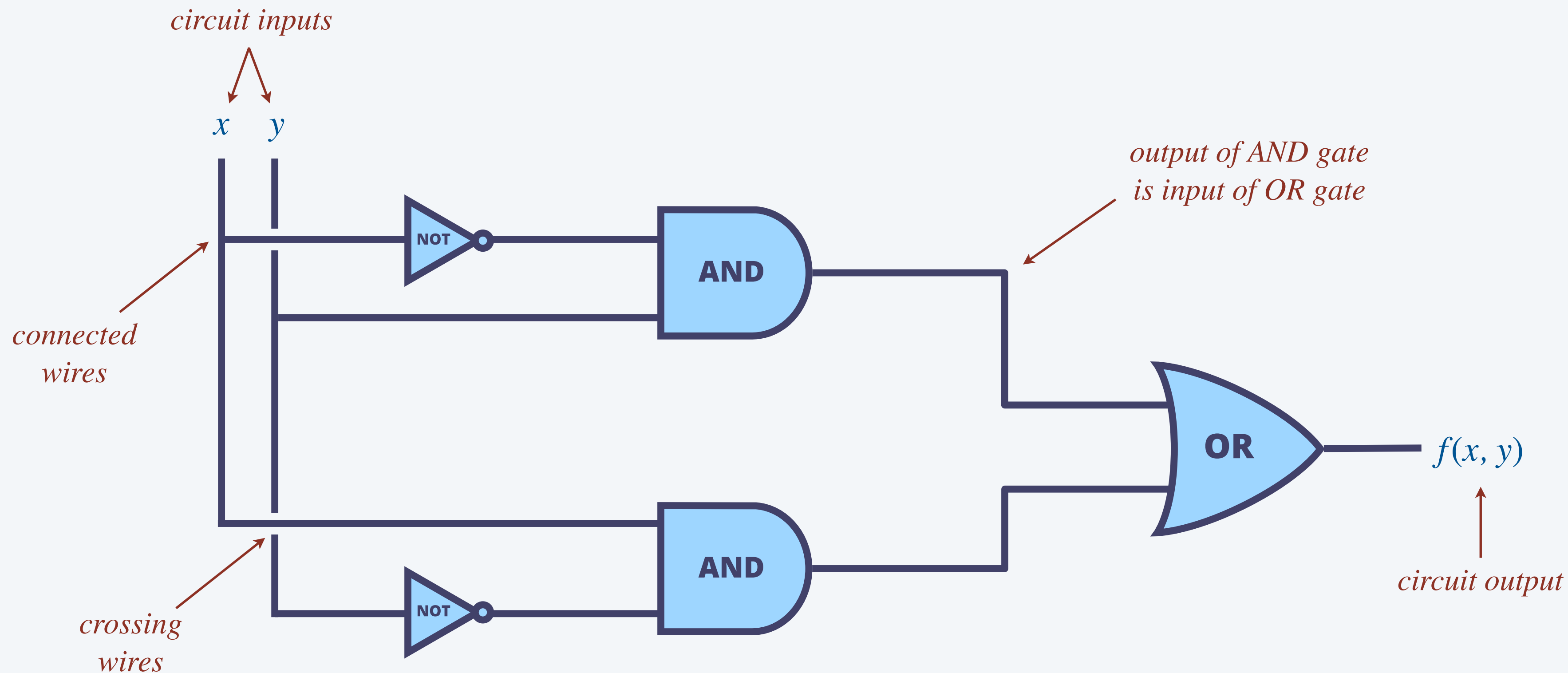- Every wire is either *on* (1) or *off* (0).
- Can connect output of one gate to input of another gate.
- Any wire connected to a wire that is *on* is also *on* (and same for *off*).




x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0



Digital circuit. A network of **logic gates** connected by **wires**.

 - Every wire is either *on* (1) or *off* (0).
- Can connect output of one gate to input of another gate.
- Any wire connected to a wire that is *on* is also *on* (and same for *off*).




x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0



For which values of x and y does the following circuit output 1 ?

 
- A. $x = 0, y = 0$
- B. $x = 0, y = 1$
- C. $x = 1, y = 0$
- D. $x = 1, y = 1$
- E. None of the above.




Multiway AND gates

Multiway AND gate.

 - 1 if all inputs are 1.
- 0 if any input is 0.



4-way AND gate symbol

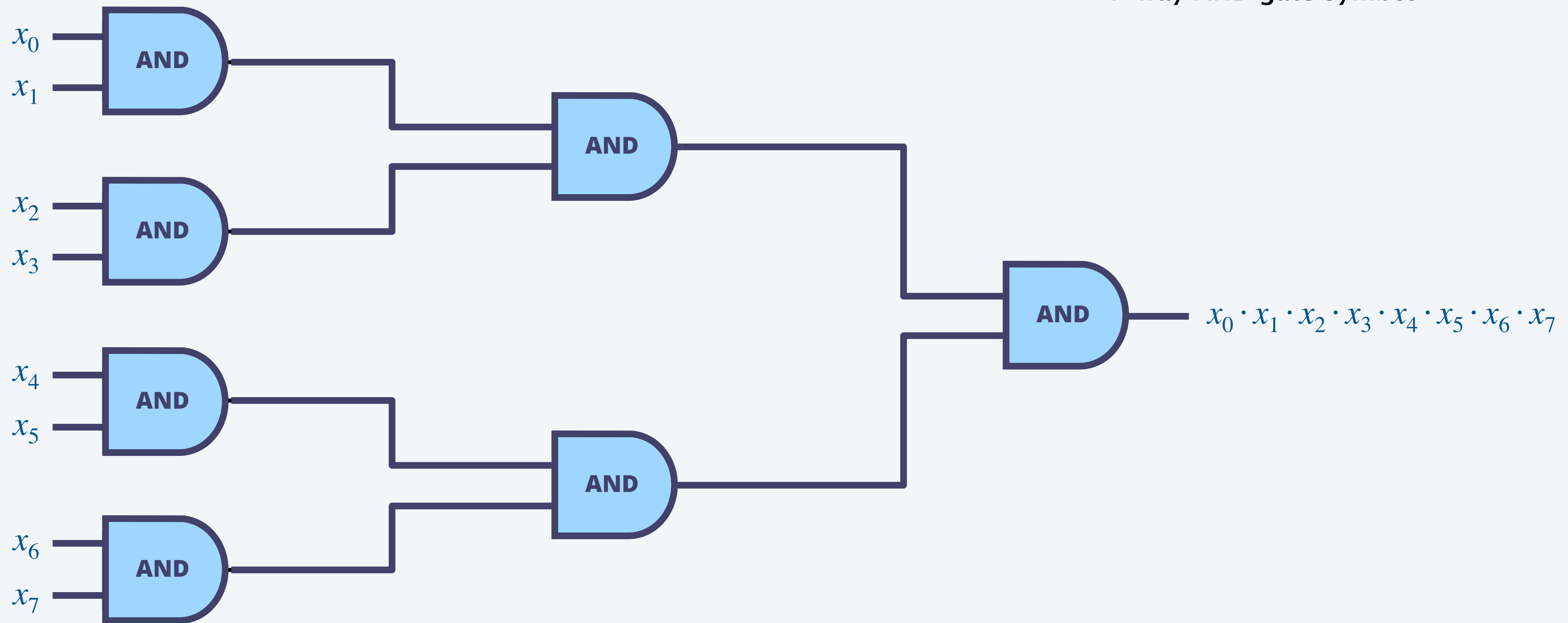


8-way AND gate implementation
(tree of 2-way AND gates)


Multiway OR gates

Multiway OR gate.

 - 1 if any input is 1.
- 0 if all inputs are 0.



4-way OR gate symbol

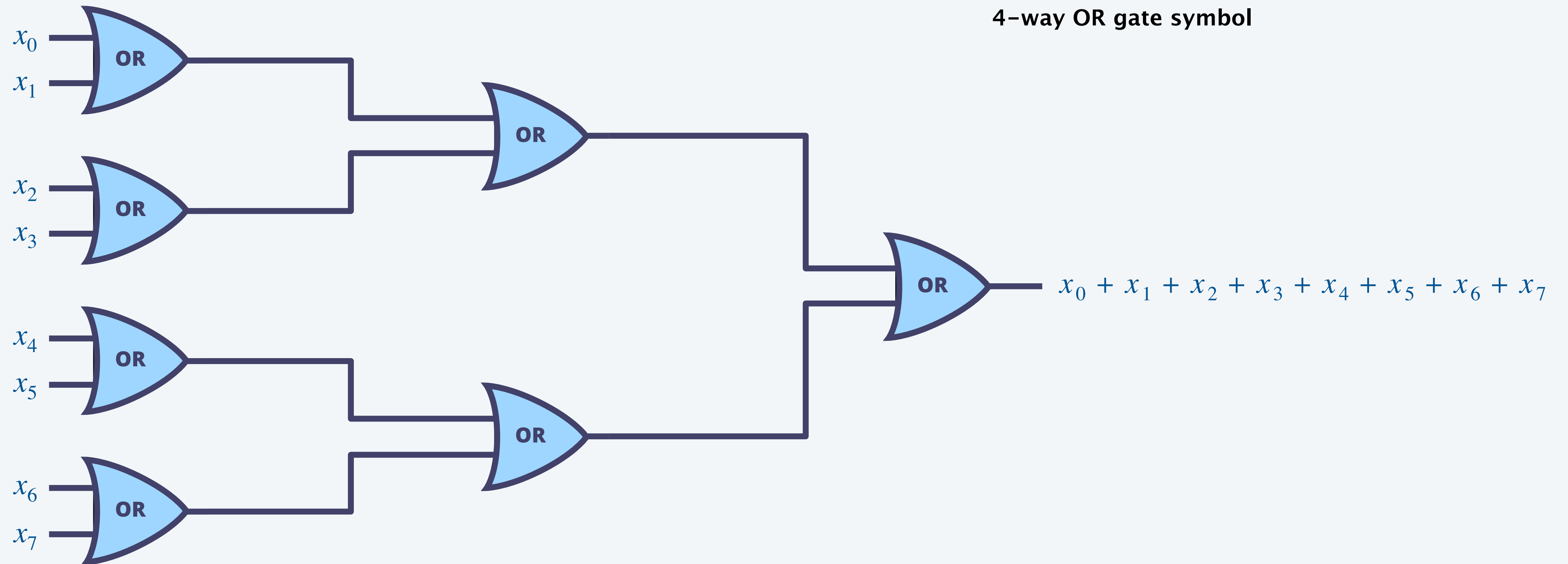


8-way OR gate implementation
(tree of 2-way OR gates)


Generalized *AND* gates

Generalized *AND* gate.

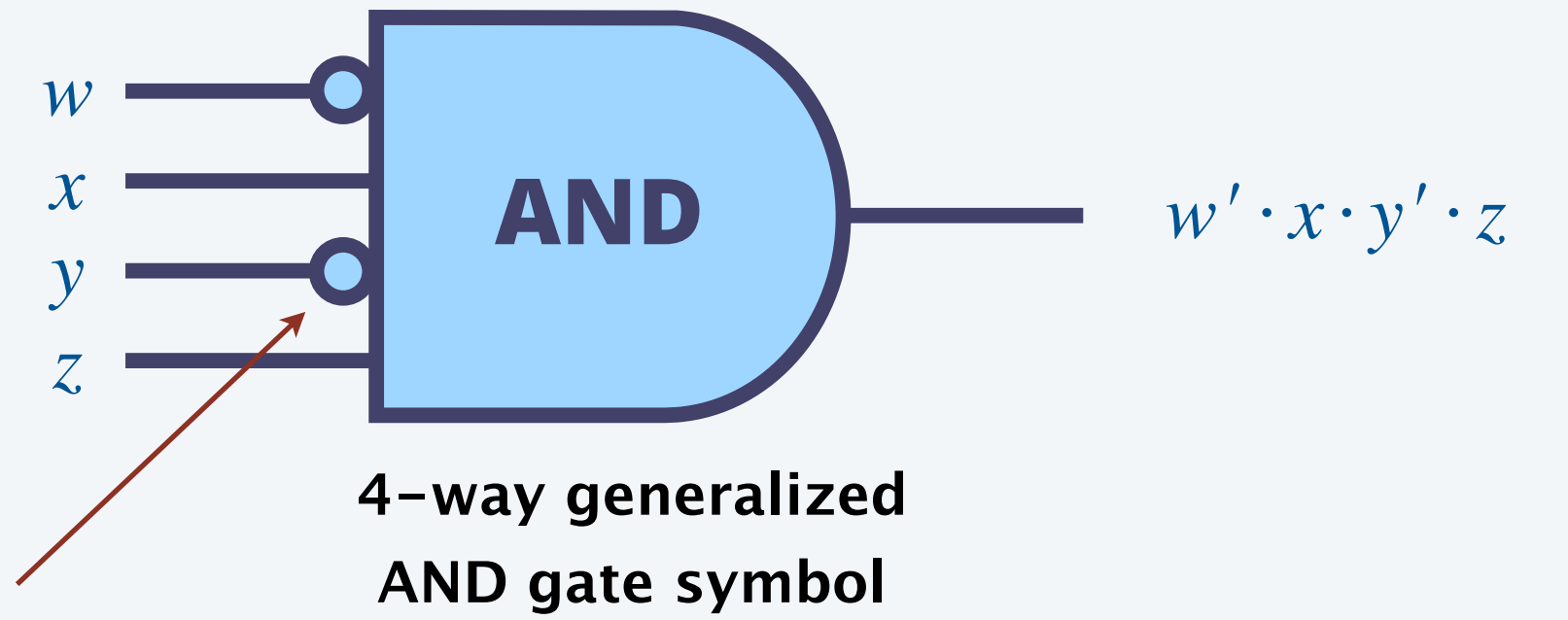- 1 for exactly one set of input values.
- 0 for all other sets of input values.



 each "inversion bubble" denotes a NOT gate



4-way generalized AND gate implementation
(tree of 2-way AND gates, plus NOT gates)

Majority function


Sum-of-products construction.

- Identify rows of truth table where the function is 1.
- Use a generalized *AND* gate for each term.
- Combine the terms using an *OR* gate.

Ex 1. Majority function.

<i>x</i>	<i>y</i>	<i>z</i>	<i>MAJ</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1 ← $x'yz$
1	0	0	0
1	0	1	1 ← $xy'z$
1	1	0	1 ← xyz'
1	1	1	1 ← xyz
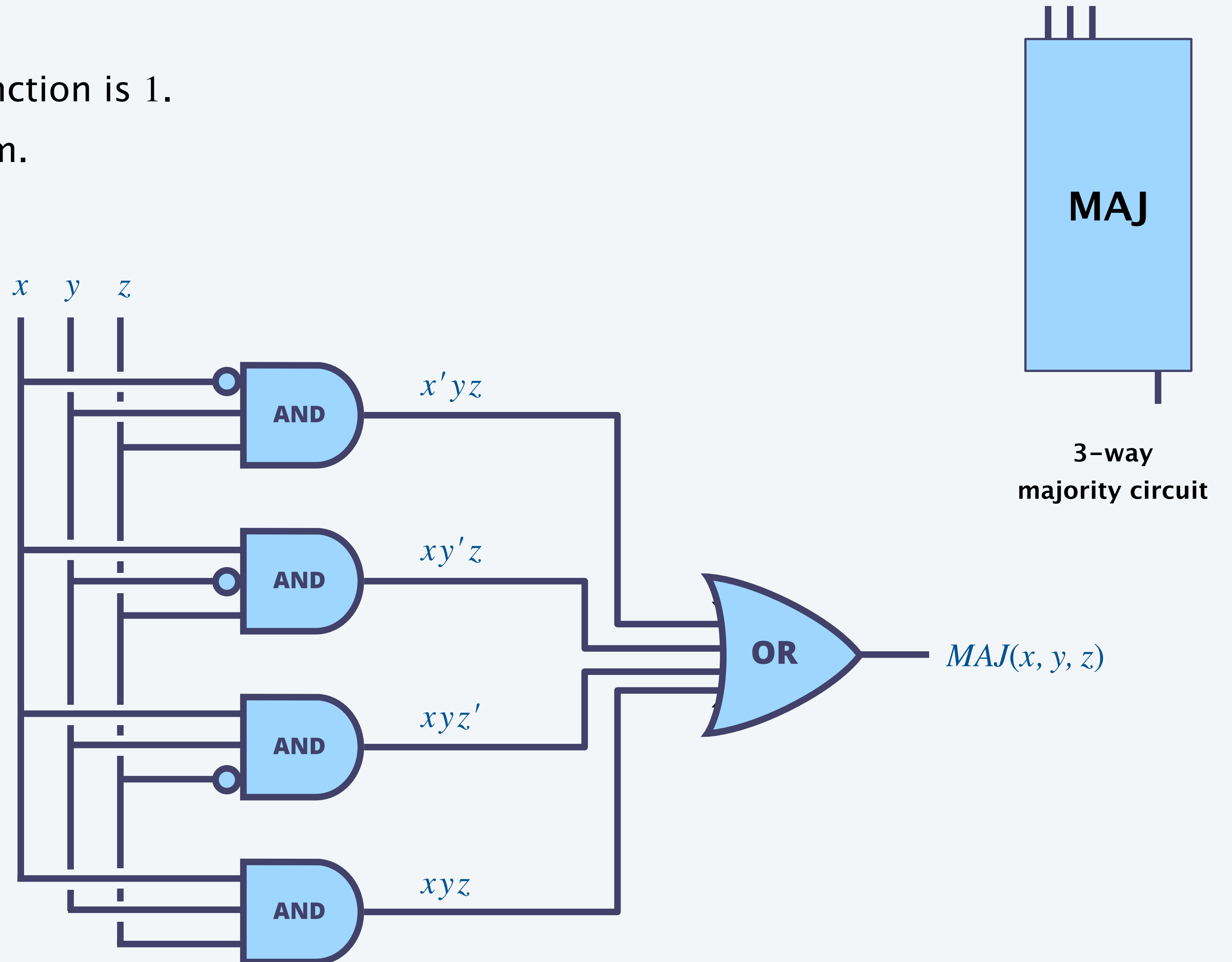
$$MAJ(x, y, z) = x'yz + xy'z + xyz' + xyz$$



Odd-parity function


Sum-of-products construction.

- Identify rows of truth table where the function is 1.
- Use a generalized *AND* gate for each term.
- Combine the terms using an *OR* gate.

Ex 2. Odd-parity function.

<i>x</i>	<i>y</i>	<i>z</i>	<i>ODD</i>
0	0	0	0
0	0	1	1 ← $x'y'z$
0	1	0	1 ← $x'yz'$
0	1	1	0
1	0	0	1 ← $xy'z'$
1	0	1	0
1	1	0	0
1	1	1	1 ← xyz
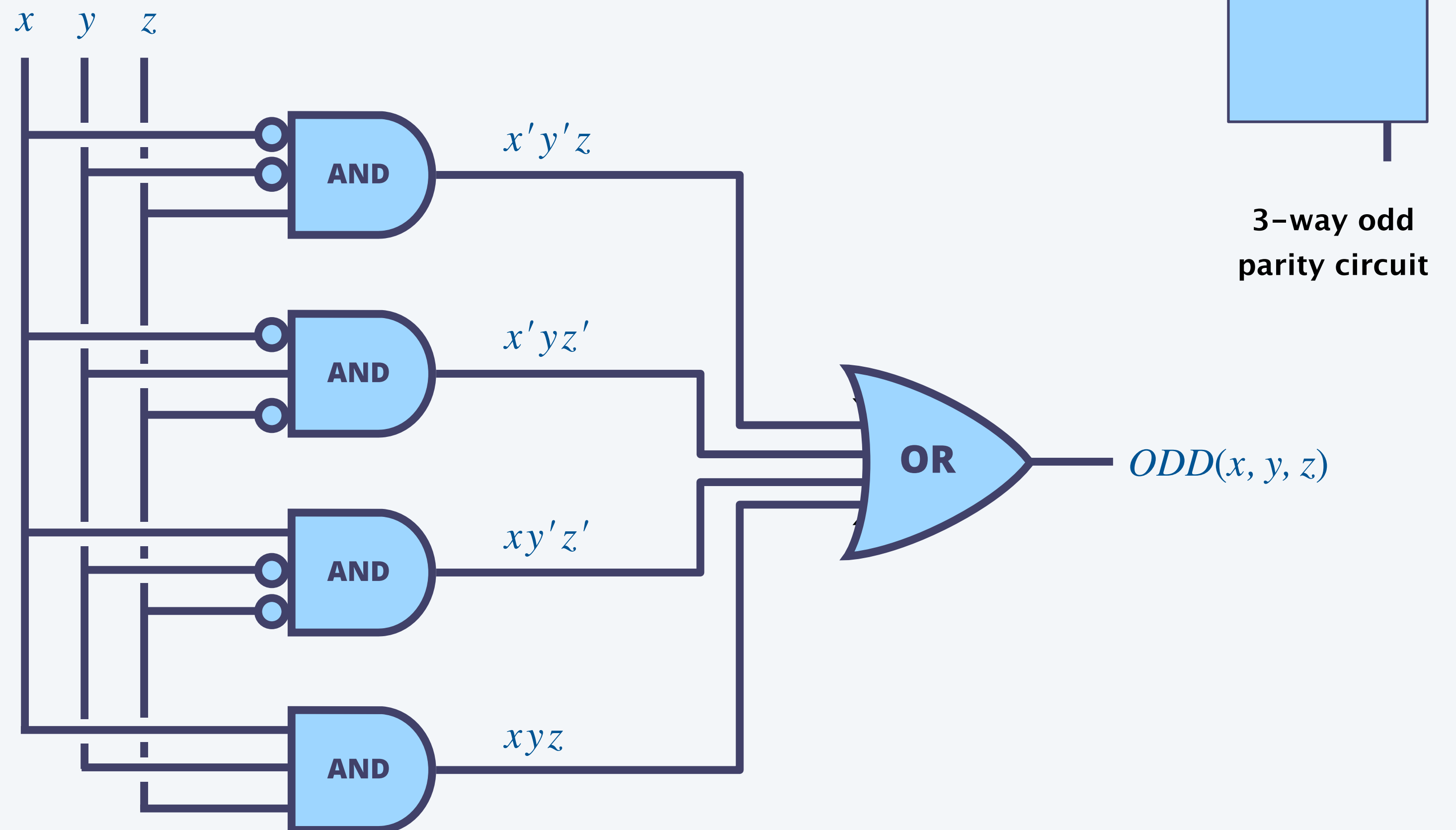
$$ODD(x, y, z) = x'y'z + x'yz' + xy'z' + xyz$$



Sum-of-products construction (summary)

Goal. Design a digital circuit that computes a given boolean function.

Recipe.

- Step 1: Represent input and output with boolean variables.
- Step 2: Construct truth table to define the function.
- Step 3: Identify rows where the function is 1.
- Step 4: Use a generalized *AND* gate for each row, and *OR* the results. ← *sum-of-products construction*

Profound consequence. Can design a digital circuit for **ANY** boolean function.


Optimized digital circuits

Caveat. Sum-of-products construction is **not optimal** in terms of:


- Space = number of gates.
- Time = depth of circuit.

← *this course: we'll ignore such low-level optimization*

Ex. Majority function.

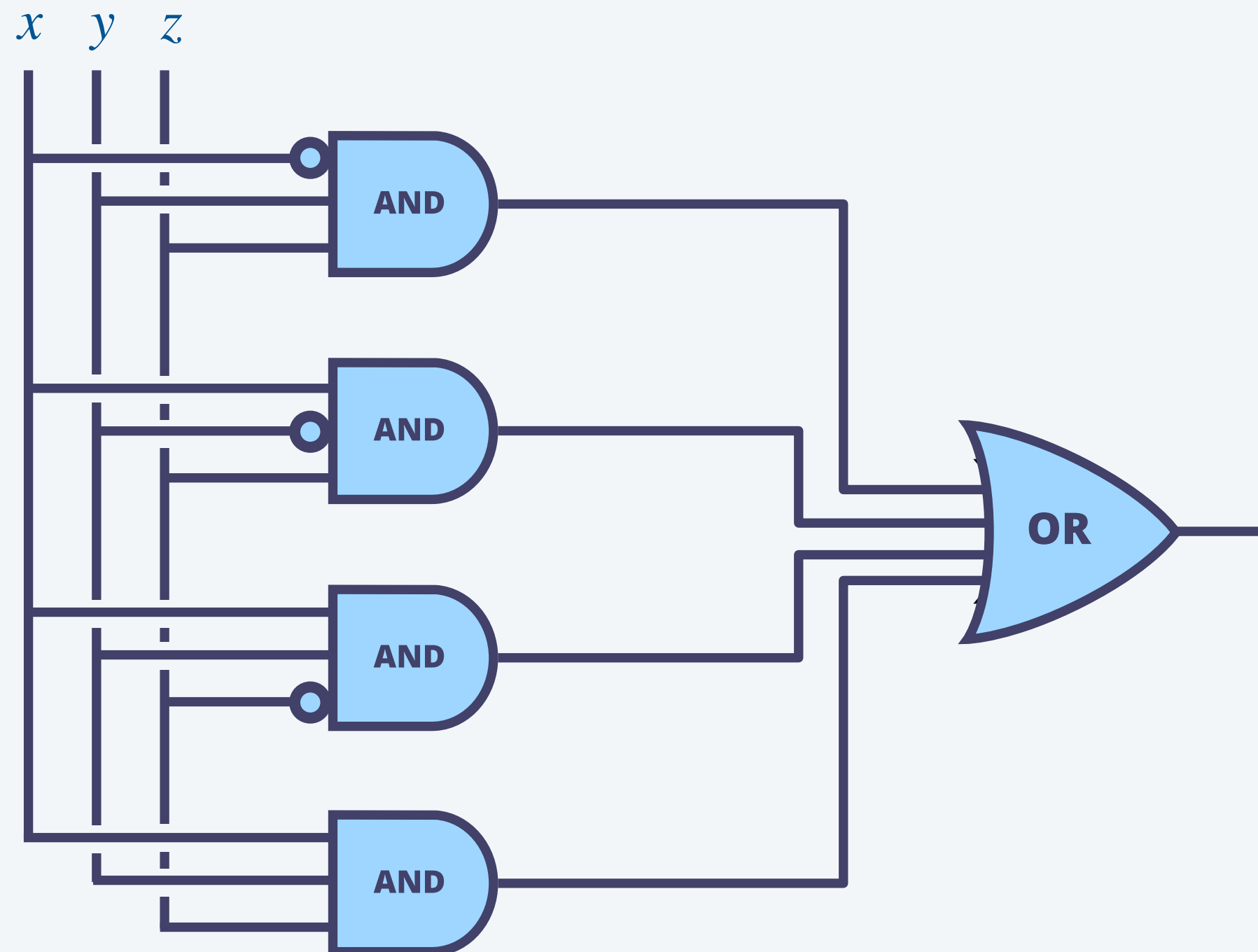

3-way majority circuit (sum-of-products)

 


3-way majority circuit (optimized)



How many 3-way generalized AND gates are needed to build the sum-of-products circuit for the following truth table?

- A. 1
- B. 2
- C. 3
- D. 4

<i>x</i>	<i>y</i>	<i>z</i>	<i>EQ</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

<https://introcs.cs.princeton.edu>

7. DIGITAL CIRCUITS


- ▶ *boolean algebra*
- ▶ *logic gates*
- ▶ *adder circuit*

Let's make an adder circuit!

Adder circuit. Compute $z = x + y$ for 4-bit binary integers. \longleftarrow *ignore integer overflow*

First step. Represent inputs and outputs in binary.
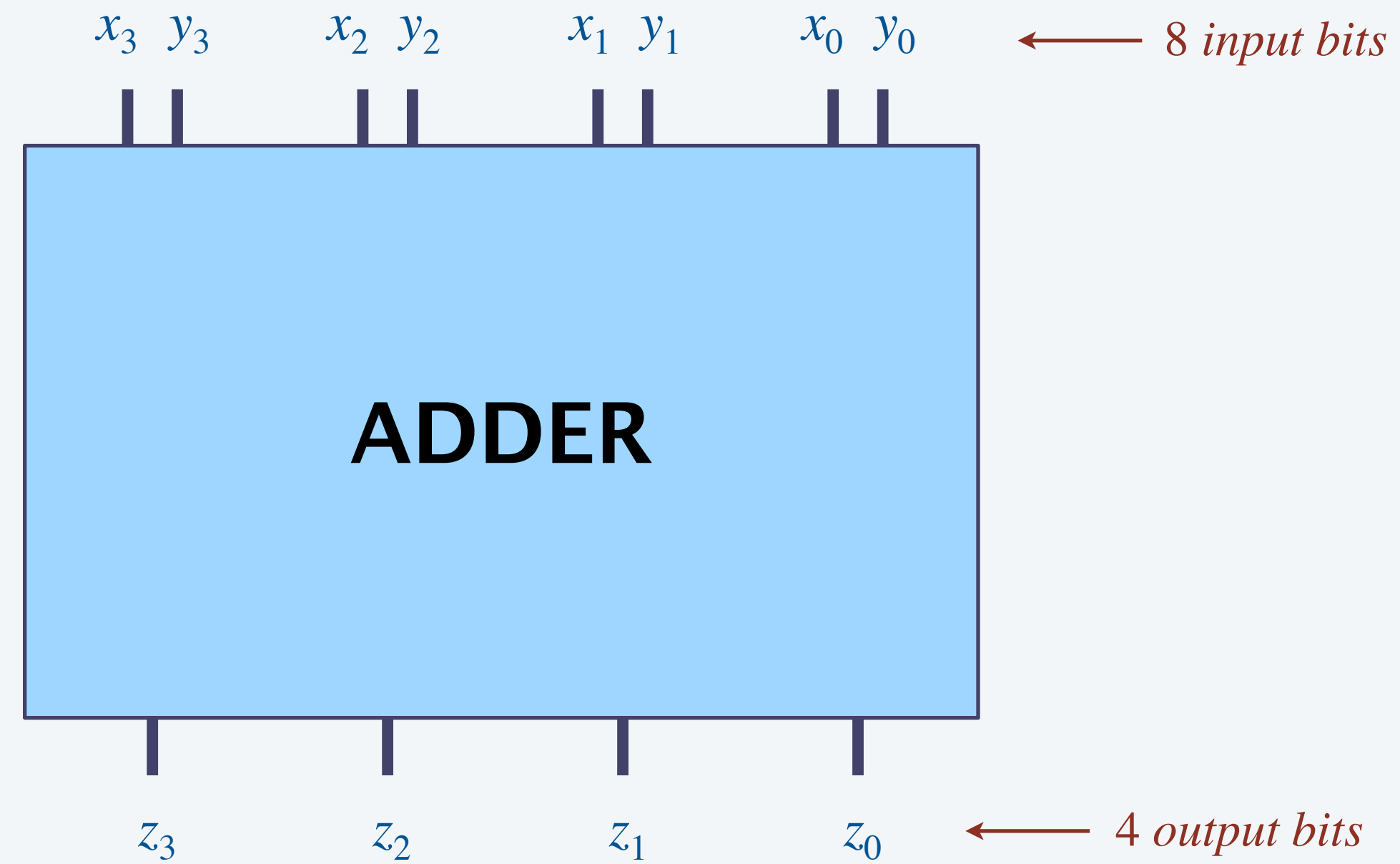
$$\begin{array}{r} x_3 \quad x_2 \quad x_1 \quad x_0 \\ + \quad y_3 \quad y_2 \quad y_1 \quad y_0 \\ \hline z_3 \quad z_2 \quad z_1 \quad z_0 \end{array}$$




Let's make an adder circuit!

Adder circuit. Compute $z = x + y$ for 4-bit binary integers. \longleftarrow *ignore integer overflow*

First step. Represent inputs and outputs in binary.
 
$$\begin{array}{r} 0101 \\ + 0110 \\ \hline 1011 \end{array}$$





What is the binary sum $1011 + 0110$?

- A. 0001
- B. 1001
- C. 1101
- D. 1121
- E. 10001

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline \end{array}$$

Let's make an adder circuit!

Adder circuit. Compute $z = x + y$ for 4-bit binary integers.

Straw-person solution. Build a truth table for each output bit.

Approach is not scalable! Truth table for 128-bit adder would have 2^{256} rows.

*exceeds number of
electrons in universe (!)*

x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	1	0	0	1	1
\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots	\vdots
1	1	1	1	1	1	1	0	1	1	0	1
1	1	1	1	1	1	1	1	1	1	1	0

truth table for 4-bit adder

Let's make an adder circuit!

Adder circuit. Compute $z = x + y$ for 4-bit binary integers.

$$\begin{array}{cccc}
 & c_3 & c_2 & c_1 & c_0 \leftarrow c_0 = 0 \\
 & x_3 & x_2 & x_1 & x_0 \\
 + & y_3 & y_2 & y_1 & y_0 \\
 \hline
 & z_3 & z_2 & z_1 & z_0
 \end{array}$$

Efficient solution. Do one bit at a time.

- Build truth table for each carry bit. \longleftarrow *majority function (!)*
- Build truth table for each sum bit.

x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

truth table for carry bit

$$c_{i+1} = MAJ(x_i, y_i, c_i)$$

Let's make an adder circuit!

Adder circuit. Compute $z = x + y$ for 4-bit binary integers.

$$\begin{array}{cccc}
 & c_3 & c_2 & c_1 & c_0 \leftarrow c_0 = 0 \\
 & x_3 & x_2 & x_1 & x_0 \\
 + & y_3 & y_2 & y_1 & y_0 \\
 \hline
 & z_3 & z_2 & z_1 & z_0
 \end{array}$$

Efficient solution. Do one bit at a time.

- Build truth table for each carry bit \leftarrow *majority function (!)*
- Build truth table for each sum bit. \leftarrow *odd-parity function (!)*

x_i	y_i	c_i	z_i	<i>ODD</i>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


truth table for sum bit

$$z_i = \text{ODD}(x_i, y_i, c_i)$$

Let's make an adder circuit!

Adder circuit. Compute $z = x + y$ for 4-bit binary integers.
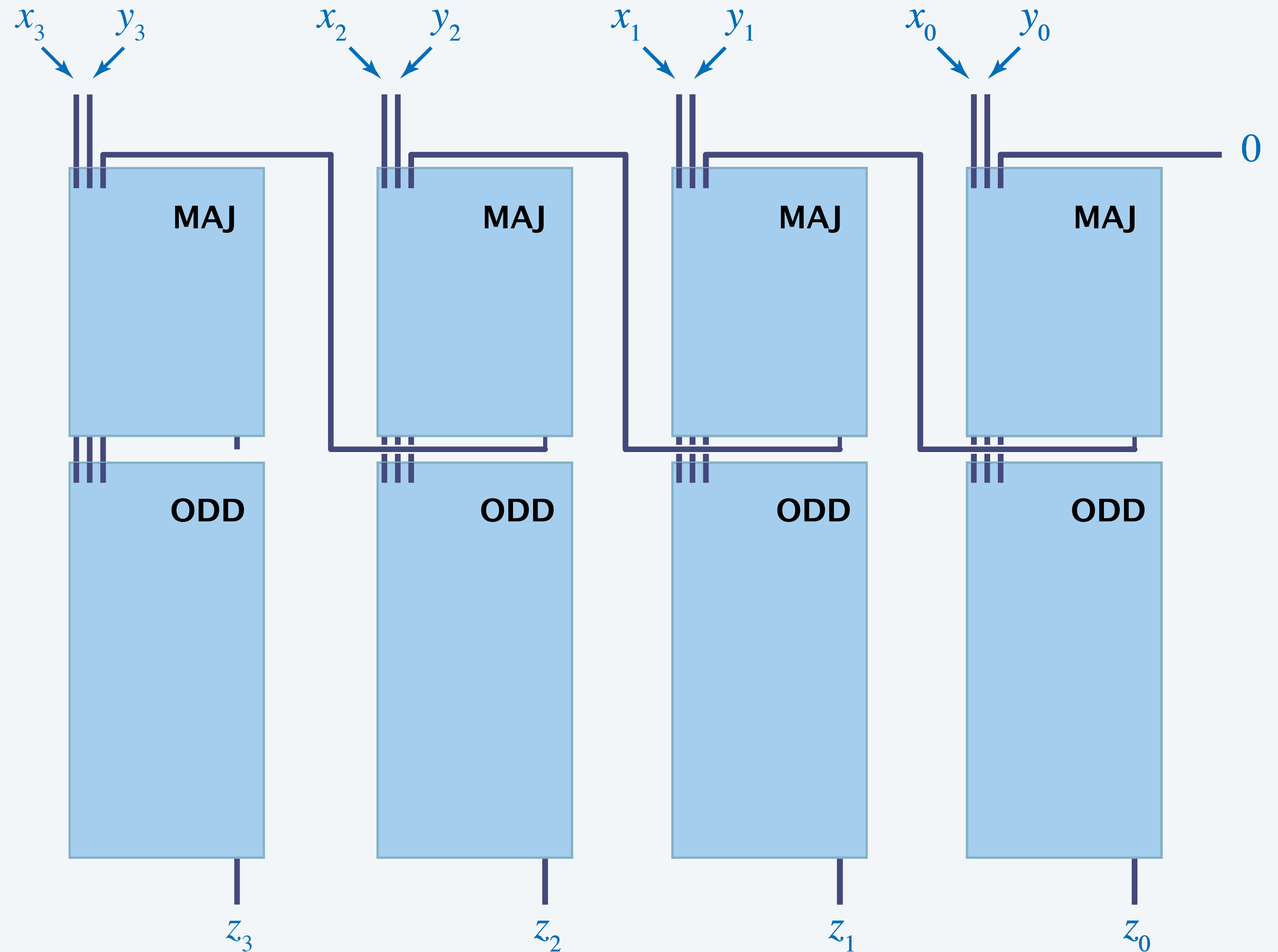
$$\begin{array}{cccc} & c_3 & c_2 & c_1 & c_0 \leftarrow c_0 = 0 \\ x_3 & x_2 & x_1 & x_0 \\ + & y_3 & y_2 & y_1 & y_0 \\ \hline z_3 & z_2 & z_1 & z_0 \end{array}$$



Efficient solution. Do one bit at a time.

- Carry bit is *MAJ*.
- Sum bit is *ODD*.
- Chain 1-bit adders to “ripple” carries.


Size of circuit. $\Theta(n)$ gates for n -bit adder.

Adder circuit trace



Circuit trace. Trace the execution of the adder circuit on a given input.

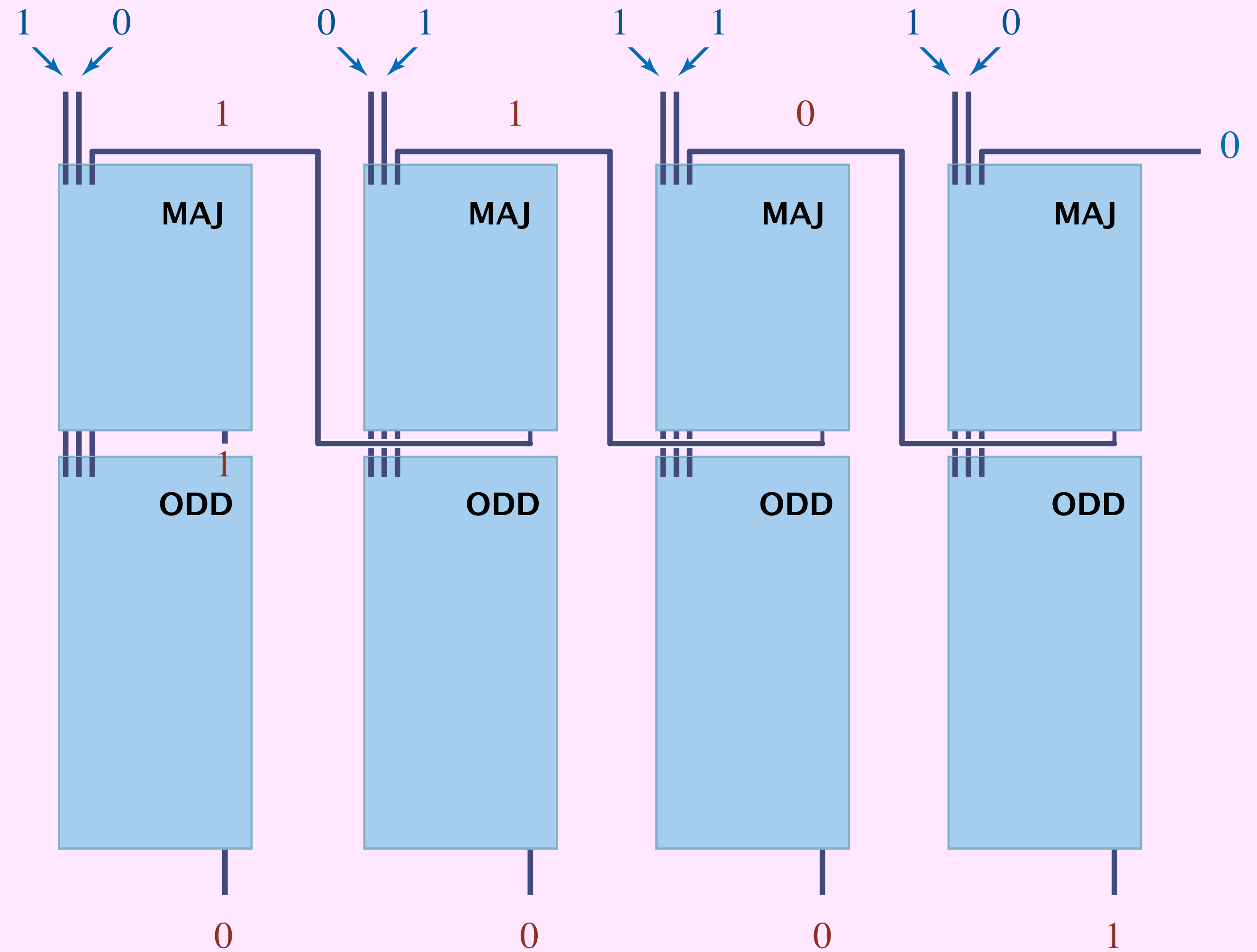
$$\begin{array}{r} 1 \quad 1 \quad 1 \\ \quad 1 \quad 0 \quad 1 \quad 1 \\ + \quad 0 \quad 1 \quad 1 \quad 0 \\ \hline 0 \quad 0 \quad 0 \quad 1 \end{array}$$



Encapsulation

Encapsulation in circuit design mirrors familiar software design principle.

 - **API** describes behavior (input and outputs) of circuit.
- **Implementation** gives details of how to build it from wires and gates.
- **Client** uses circuit as a black box.




Bottom line. We manage complexity by **encapsulating** circuits.

Layers of abstraction

Layers of abstraction apply with a vengeance.

- On/off.
- Switch.
- Primitive gates (*AND*, *OR*, *NOT*).
- Composite gates (multiway *AND/OR*, *MAJ*, *ODD*).
- Adder circuit.
- Memory.
- Arithmetic logic unit (ALU).
- Central processing unit (CPU).
- Input and output.
- Your computer.

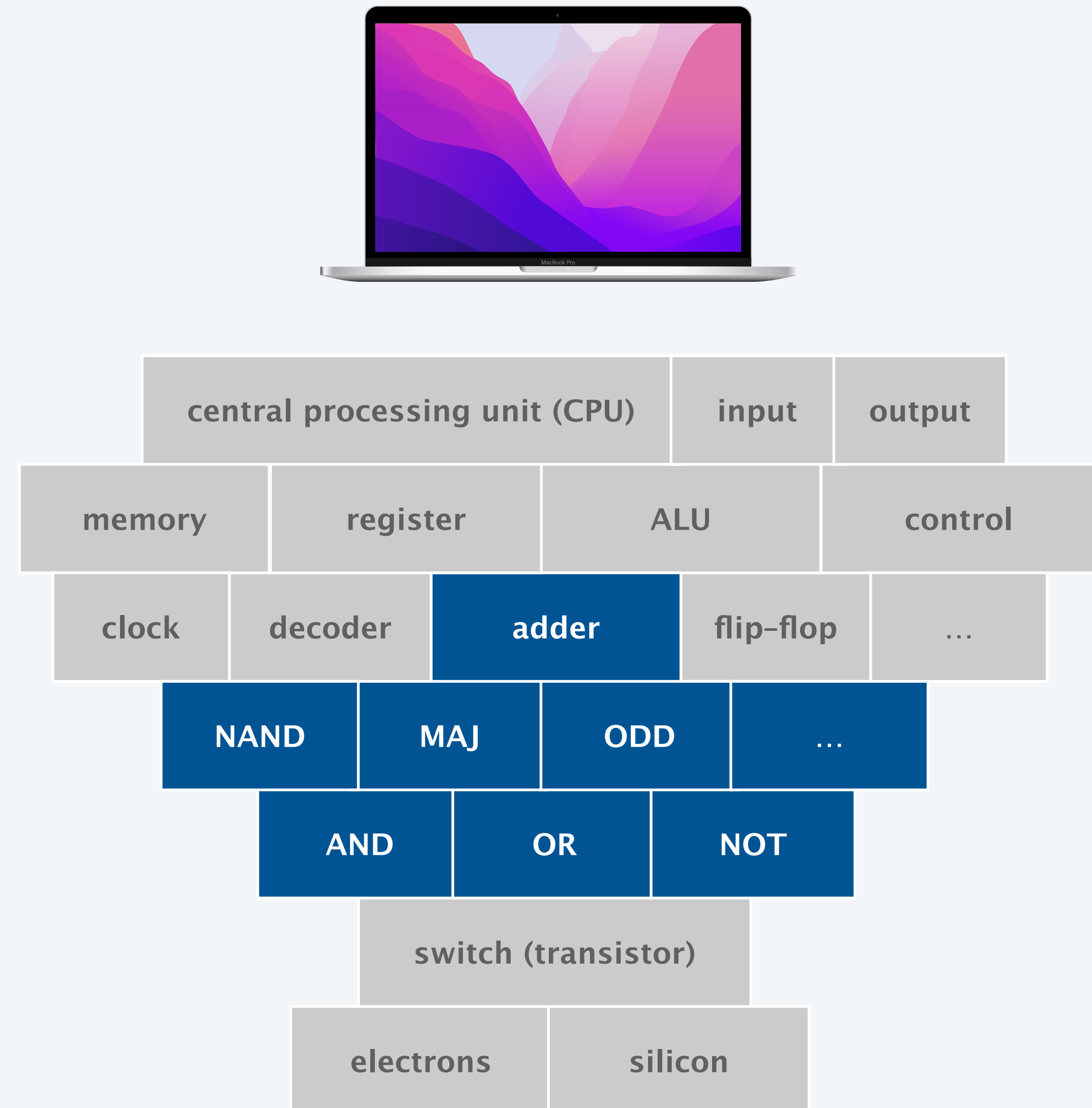Want to learn more? See ECE 206 and ECE 365.





Co-instructors, course admin, and graduate student preceptors.



Alan Kaplan



Sebastian Caldas



Kobi Kaplan

Undergrad graders and lab TAs. Apply to be one next semester!

A final thought

Credits

image	source	license
<i>Retro Telephone and Smartphone</i>	<u>Adobe Stock</u>	<u>education license</u>
<i>Macbook Pro</i>	<u>Apple</u>	
<i>Samsung Galaxy S23</i>	<u>Samsung</u>	
<i>Xbox One</i>	<u>Microsoft</u>	
<i>Cardiac Pacemaker</i>	<u>Adobe Stock</u>	<u>education license</u>
<i>Apple A16 Bionic Chip</i>	<u>Apple</u>	
<i>Boole is Coole</i>	<u>IrishPhilosophy</u>	<u>CC BY-NC-SA 2.0</u>
<i>Boole Orders Lunch</i>	<u>Sidney Harris</u>	
<i>From NAND to Tetris</i>	<u>nand2tetris.org</u>	

Credits

image	source	license
<i>Claude Shannon</i>	<u>Lucent Technologies</u>	
<i>Bit Player Theatrical Poster</i>	<u>thebitplayer.com</u>	
<i>John Hutton as Claude Shannon</i>	<u>thebitplayer.com</u>	
<i>Logic Gate Symbols</i>	<u>Adobe Stock</u>	<u>education license</u>
<i>Apple MacBook Pro</i>	<u>Adobe Stock</u>	<u>education license</u>