



Sequential and Clocked Circuits; Finite State Machines

3/28/2006

COS 116

Instructor: Sanjeev Arora


Sequential Circuits (Recap.)

- Circuits with AND, OR and NOT gates.
- Cycles *are* allowed.
- Can exhibit “memory”.
- May exhibit instabilities (saw last time).

Recap: D Flip Flop


a.k.a. “Airlock”, “Master-Slave”

Basic Memory Block – stores 1 bit.

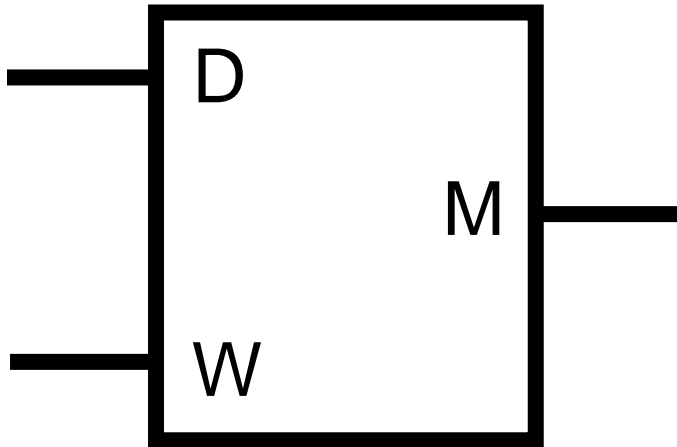

If we “toggle” the write input (setting it 1 then setting it 0) then M acquires the value of D.

Timing Diagram

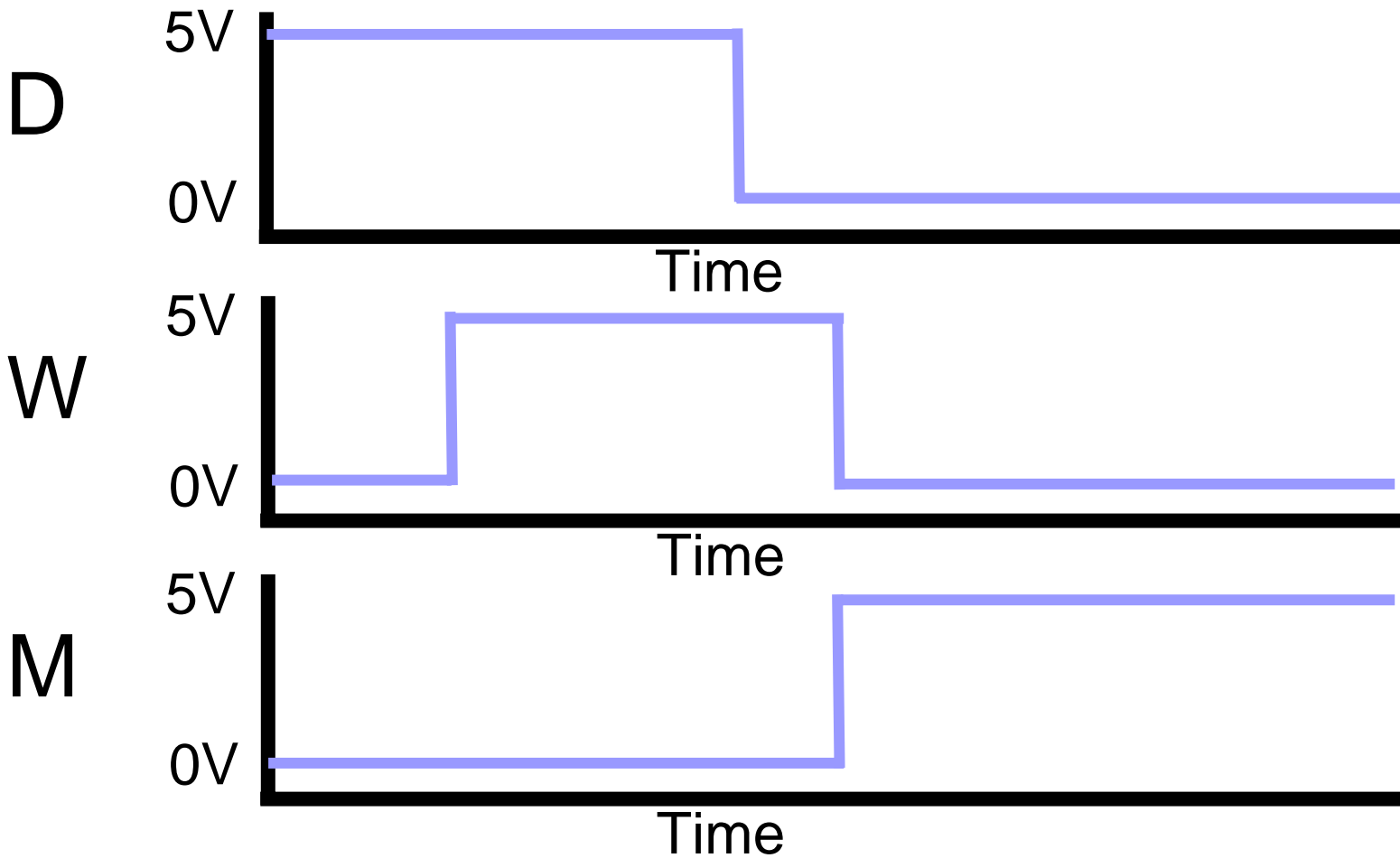

What controls the “Write” signal?


- Often, the system clock!
- “clock” = device that sends out a fluctuating voltage signal that looks like this




“Computer speed” often refers to the clock frequency (e.g. 2.4GHz)

Synchronous Sequential Circuit

(aka Clocked Sequential Circuit)

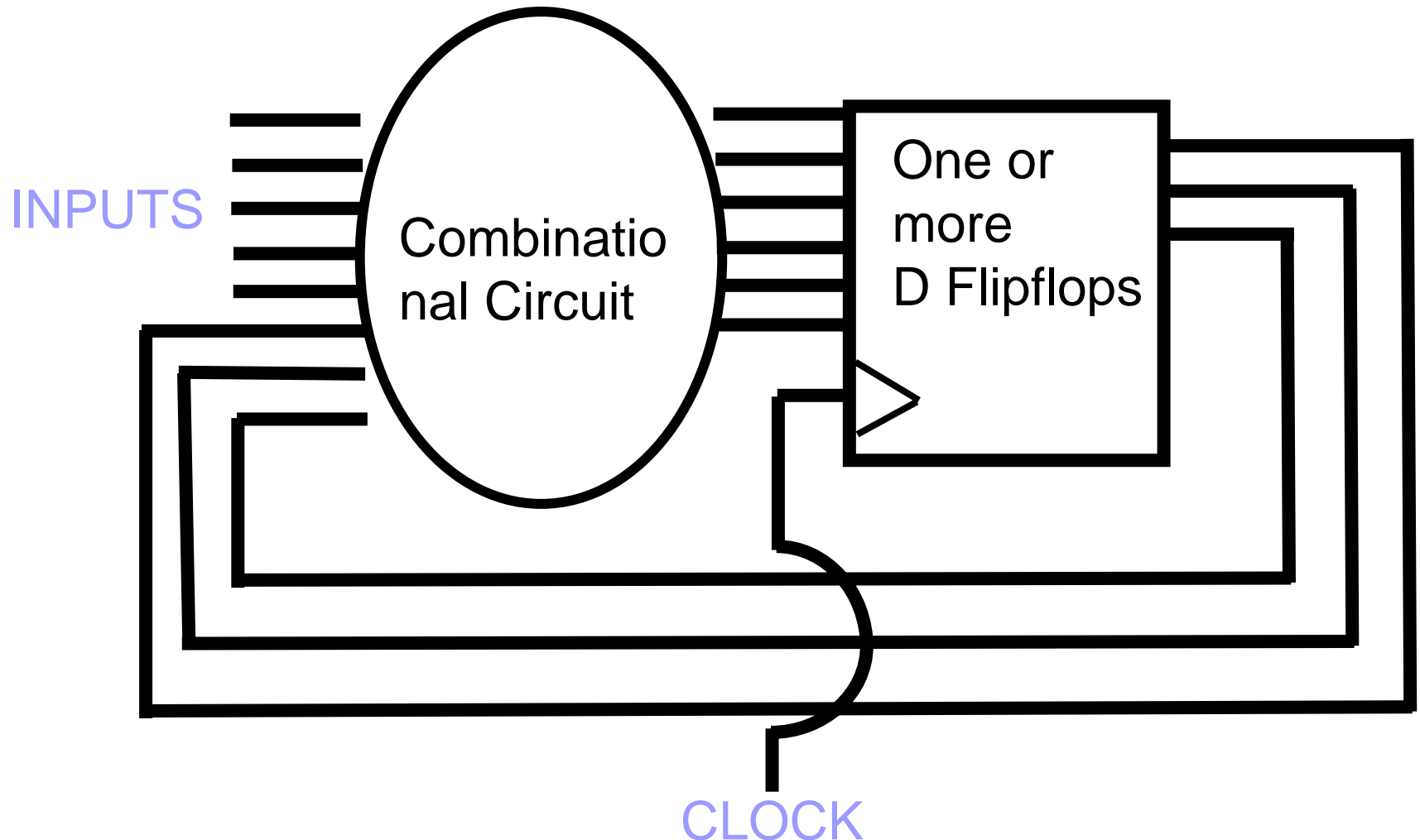

Shorthands

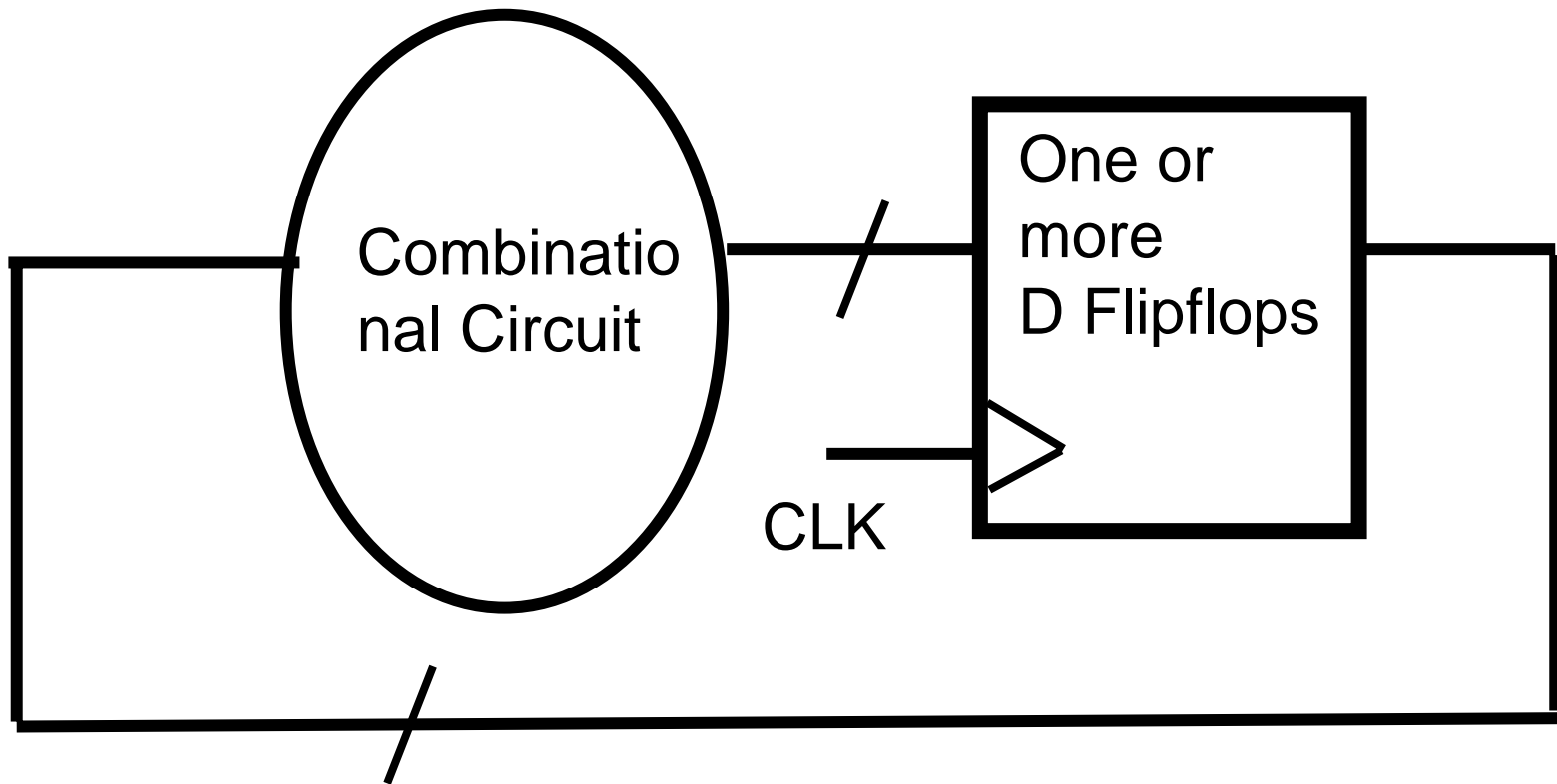

Clock Speeds



Heinrich Hertz
1857-94

1974	Intel 8080	2 MHz (Mega = Million)
1981	Original IBM PC	4.77 MHz
1993	Intel Pentium	66 MHz
2005	Pentium 4	3.4 GHz (Giga = Billion)

Distance traveled by light during 1 clock cycle of Pentium 4
4 inches




What limits clock speed?




Finite State Machines

State diagram for automatic door

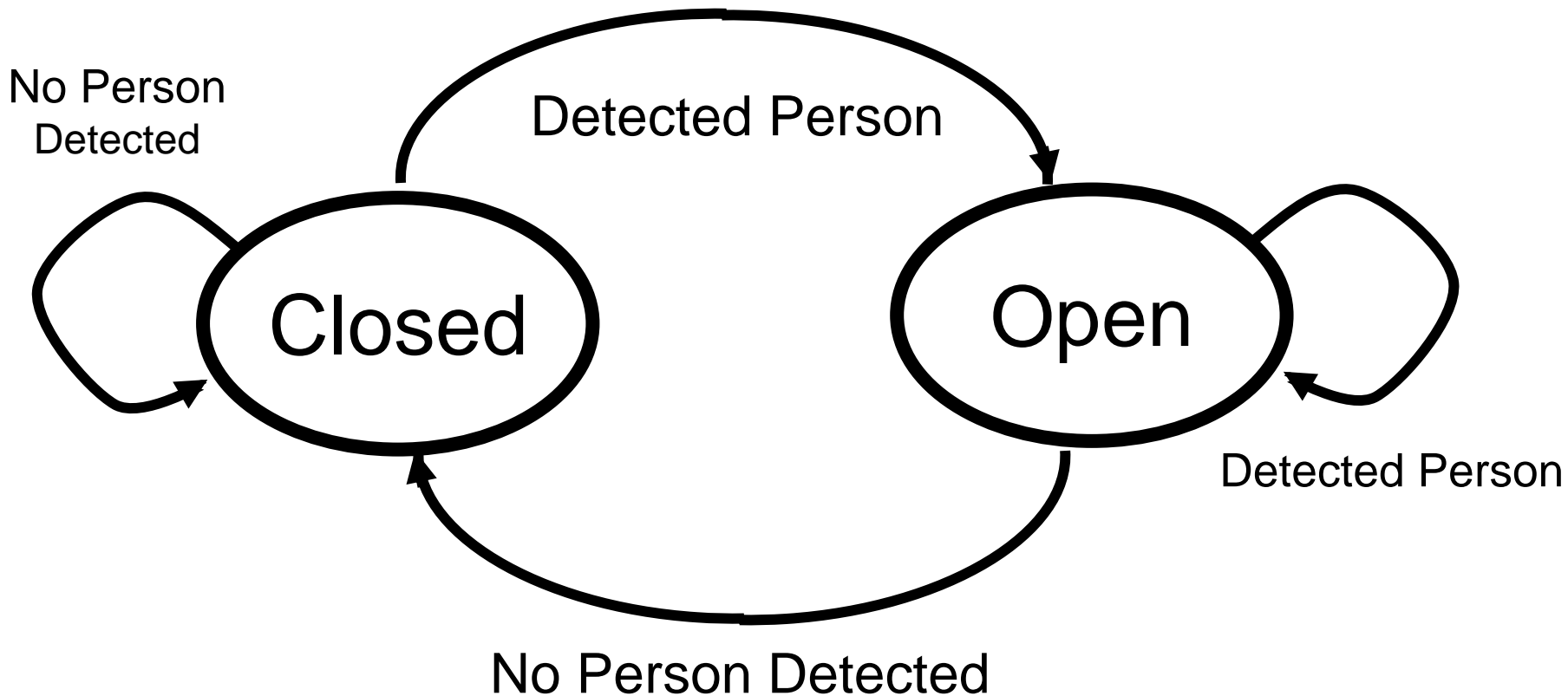

Implementing as synchronous circuit

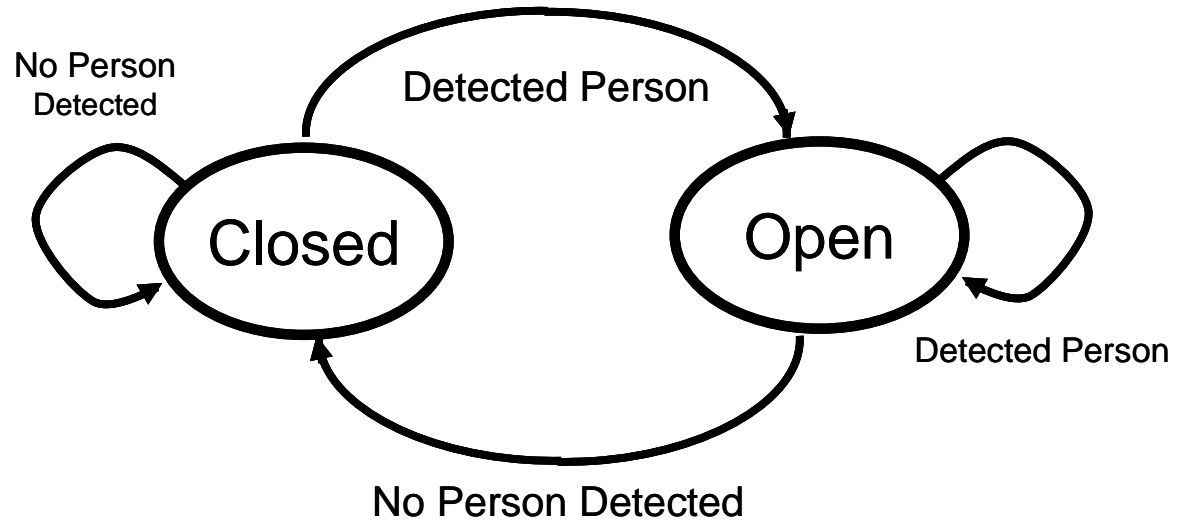

INPUT


0 = No Person Detected
1 = Person Detected

STATE


0 = Door Closed
1 = Open

Input	Present State	Next State
0	0	0
1	0	1
0	1	0
1	1	1

Implementation

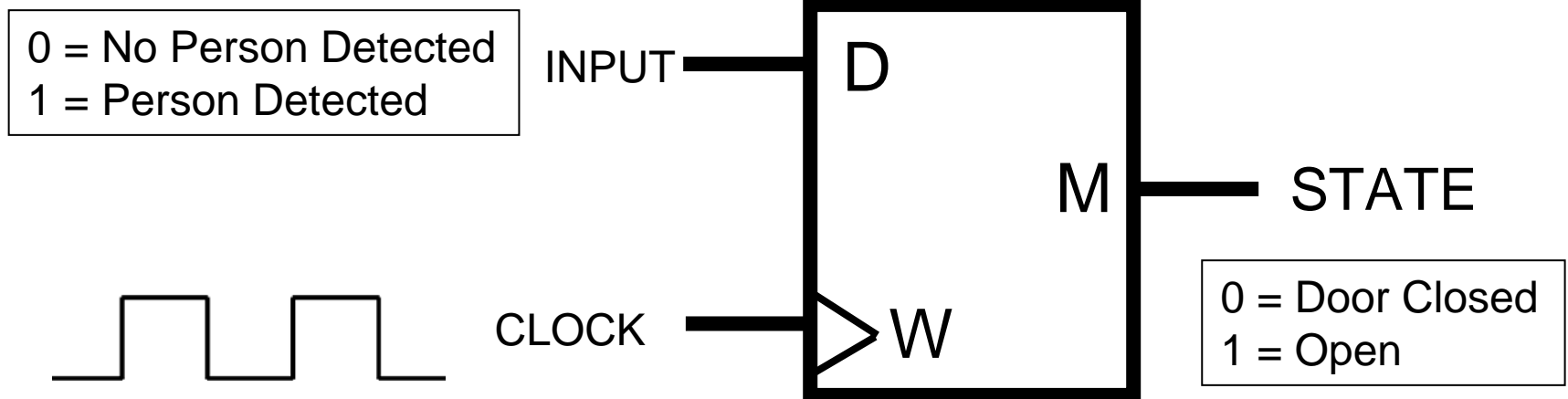

Moore FSM (see handout)

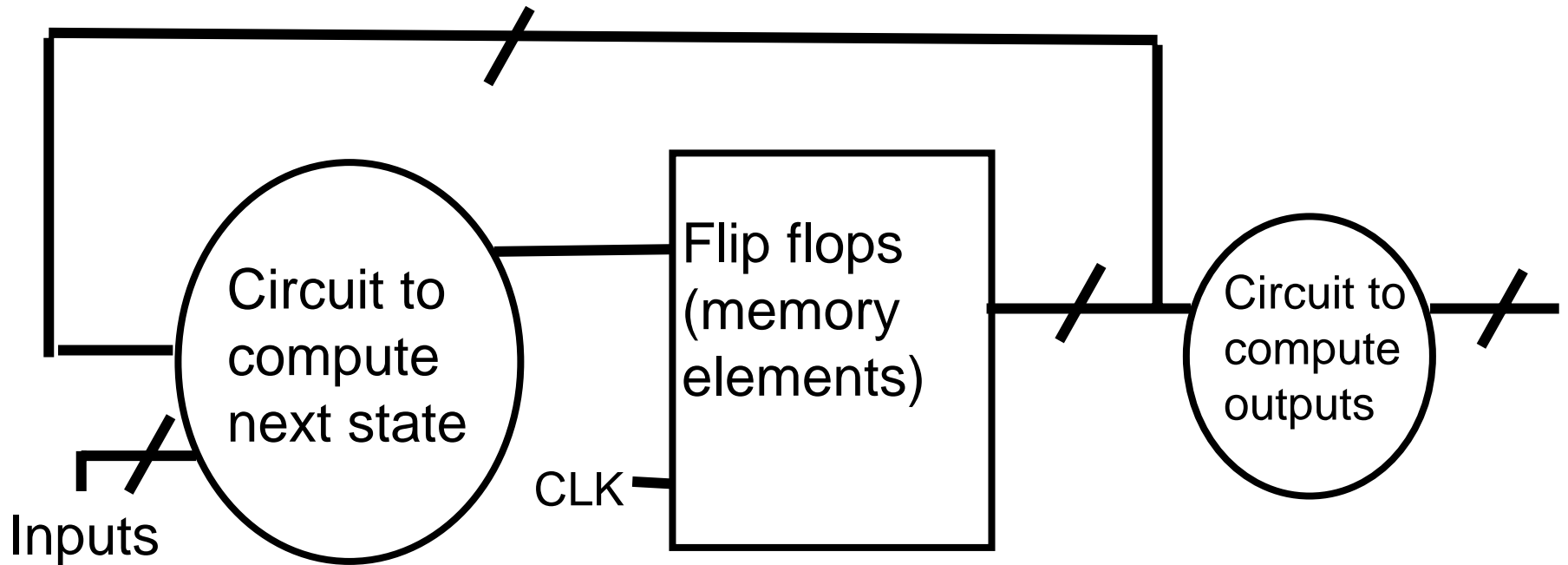

K Flip flops allow FSM to have 2^K states

Other examples of FSMs

- Sisyphus




- Brook's Genghis (51 FSMs) (see p. 46 in our text)



- Human Soul a la Aquinas (see Handout)

Portion of Genghis AFSM Network

[Parker'94]

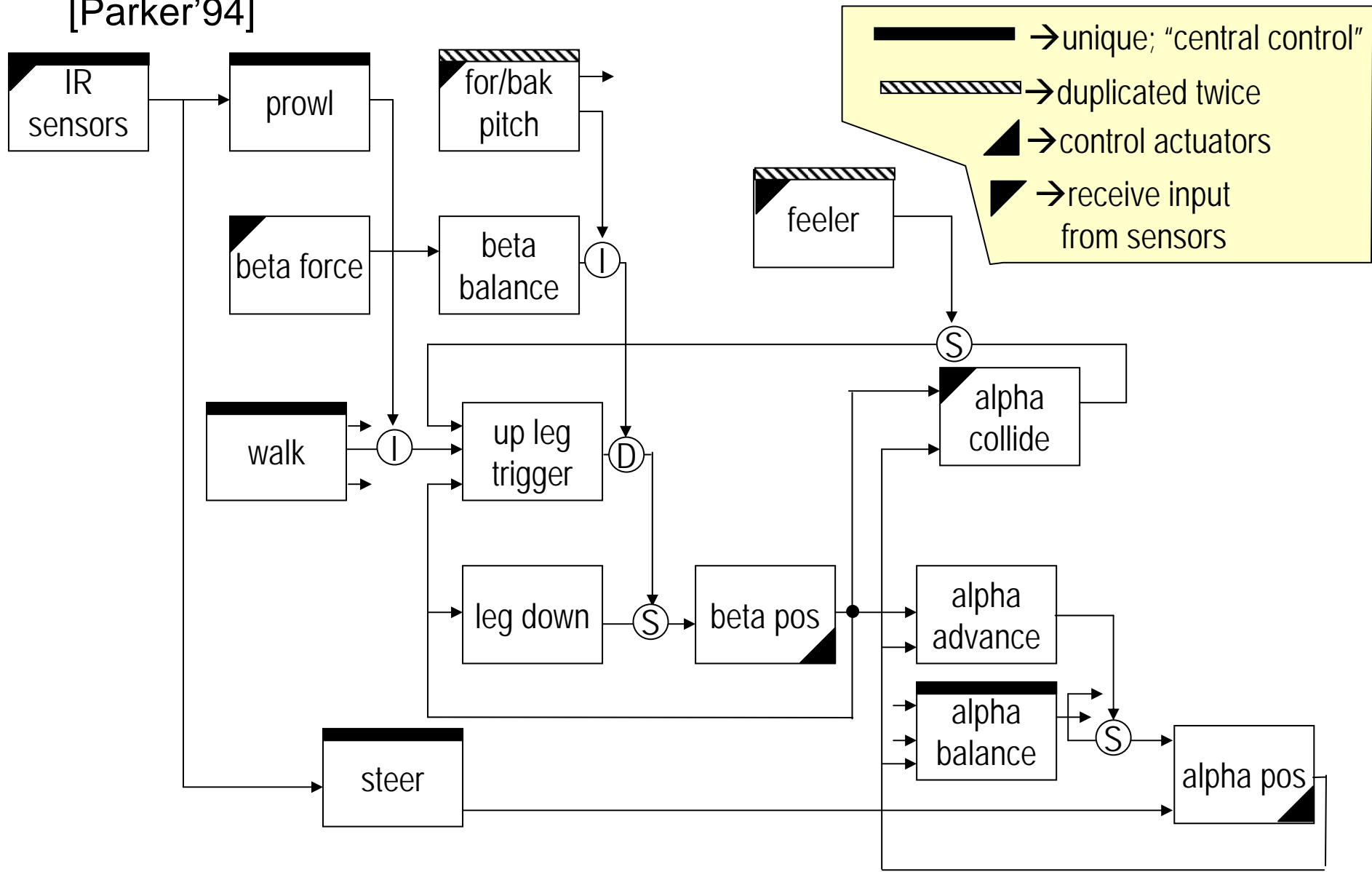



Finally...

How computers execute programs.

Scribbler Control Panel Program

```
If <Obstacle on Either Side> Then
{
  Play Sound for 1s at Frequency 440Hz
}
Else
{
  LED: ON, ON, ON
}
END
```

F5



**“Download to Robot”
(Compilation)**

Machine Executable Code

Funduc Software Hex Editor - [t1.gif]


File Edit View Bookmarks Window Help


000000	47	49	46	38	39	61	14	00	0f
000009	00	b3	08	00	ff	60	00	cf	60
000012	00	cf	2f	00	cf	60	2f	ff	90
00001b	2f	90	2f	00	60	2f	00	ff	60
000024	2f	ff	ff	ff	00	00	00	00	00
00002d	00	00	00	00	00	00	00	00	00
000036	00	00	00	00	00	00	00	21	ff
00003f	0b	4e	45	54	53	43	41	50	45
000048	32	2e	30	03	01	00	00	00	21
000051	f9	04	09	14	00	08	00	2c	00
00005a	00	00	00	14	00	0f	00	00	04
000063	55	10	c9	49	ab	9d	26	eb	9d
00006c	af	19	44	28	8e	81	51	19	42

Meet the little green man..



The Fetch – Decode – Execute FSM

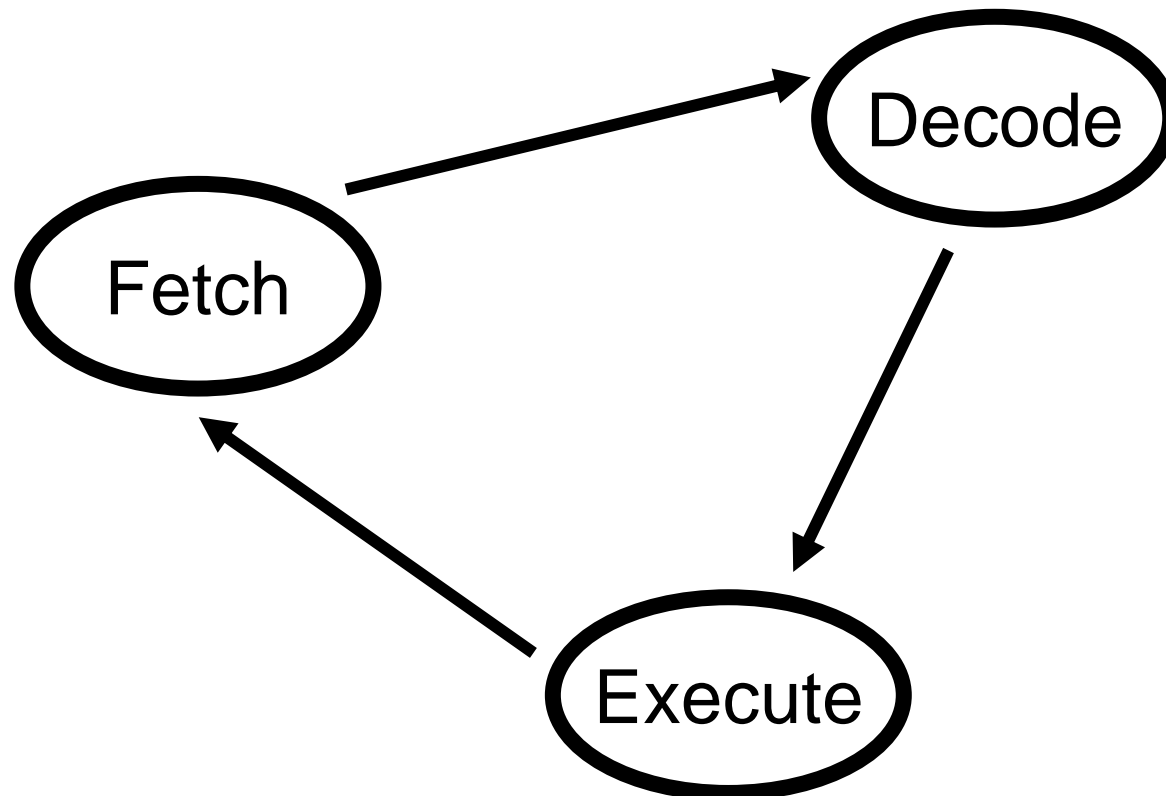

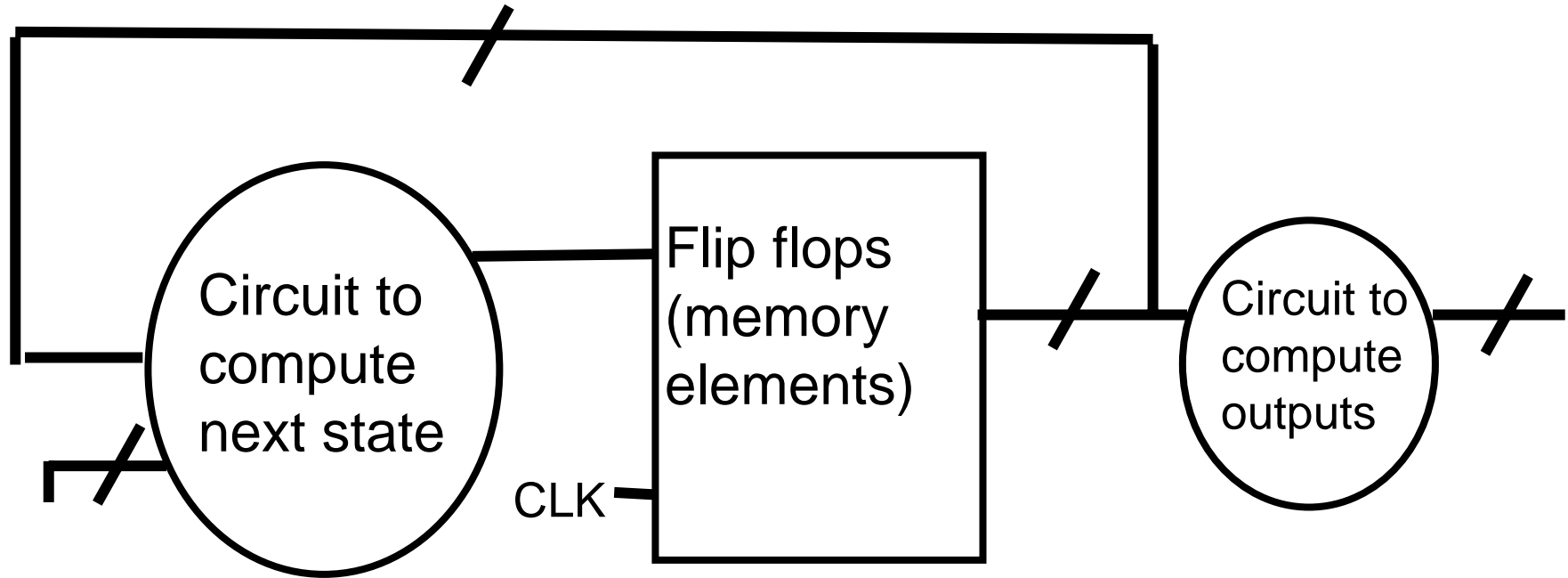

.....0110100000110111101010111.....

Program stored in machine memory; each instruction represented by say 64 bits

Discussion: How would you implement a Turing-Post program with a digital circuit?

...	0	0	0	0	0	0	1	1	1	1	0	0	0	0	0	0	0	0	...
-----	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	-----

1. PRINT 0
2. GO RIGHT
3. GO TO STEP 1 if 1 SCANNED
4. GO TO STEP 1 if 0 SCANNED
5. STOP

Assume "PRINT" and "SCAN" as basic operations