



Memory; Sequential & Clocked Circuits; Finite State Machines

COS 116, Spring 2010


Adam Finkelstein

Recap: Boolean Logic

Boolean Expression

$$E = S \text{ AND } \bar{D}$$

Boolean Circuit

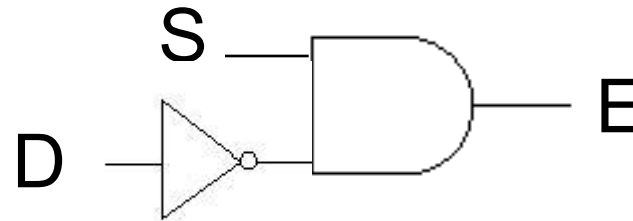

Truth table:


Value of E for every possible D, S.

TRUE=1; FALSE= 0.

| D | S | E |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Truth table has 2^k rows if the number of variables is k

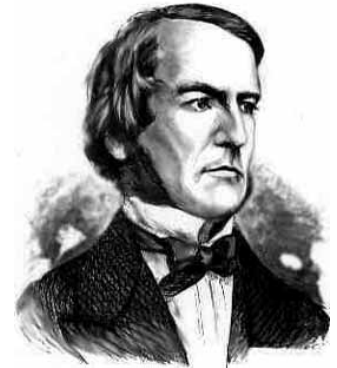Boole's reworking of Clarke's "proof" of existence of God (see handout)



- General idea: Try to prove that Boolean expressions E_1, E_2, \dots, E_k cannot simultaneously be true
- Method: Show $E_1 \cdot E_2 \cdot \dots \cdot E_k = 0$
- Discussion: What exactly does Clarke's "proof" prove? How convincing is such a proof to you?

Also: Do Google search for "Proof of God's Existence."

Combinational circuit for binary addition?

$$\begin{array}{r} 25 \qquad 11001 \\ + 29 \qquad 11101 \\ \hline 54 \qquad 110110 \end{array}$$

- Want to design a circuit to add any two N -bit integers.

Is the truth table method useful for $N=64$?

Modular design


Have small number
of basic components.

Put them together to achieve
desired functionality

Basic principle of modern industrial design;
recurring theme in next few lectures.




1-bit adder

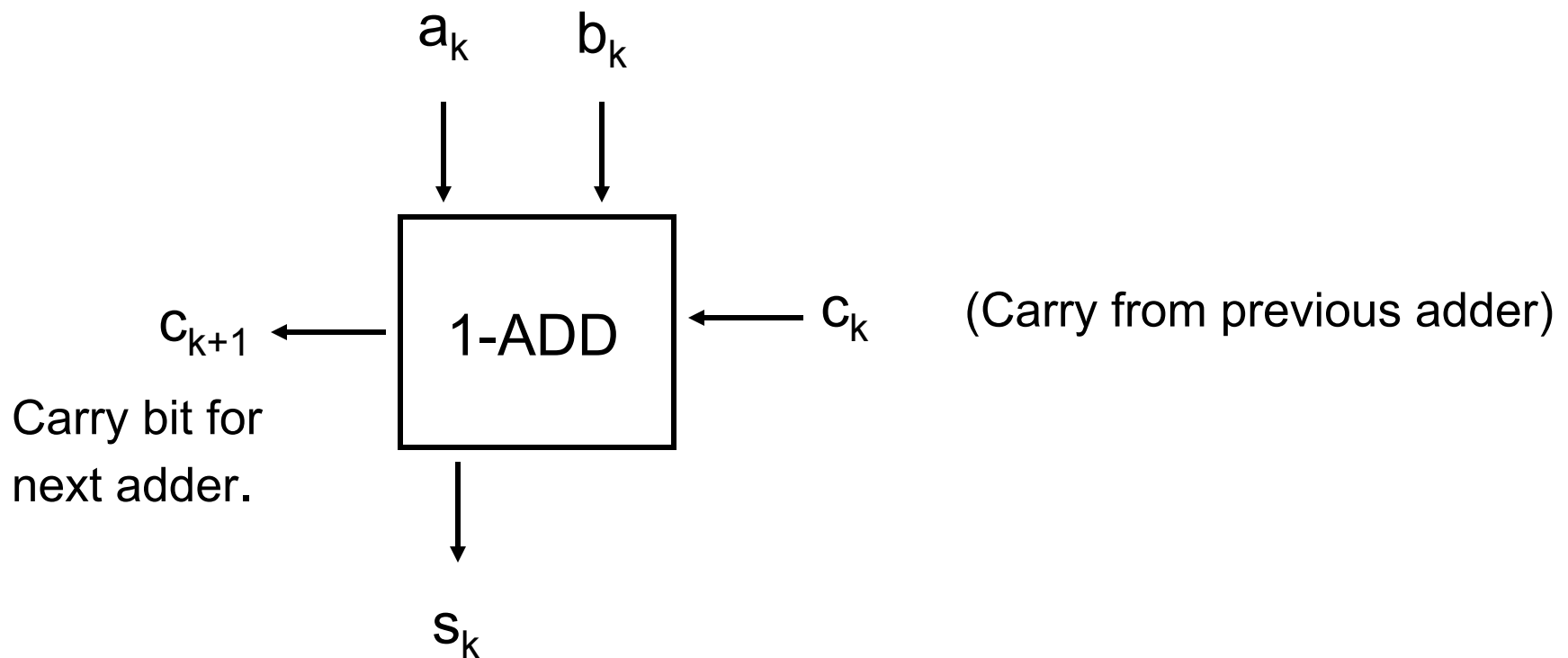



Do yourself: Write truth table, circuit.

A Full Adder (from handout)

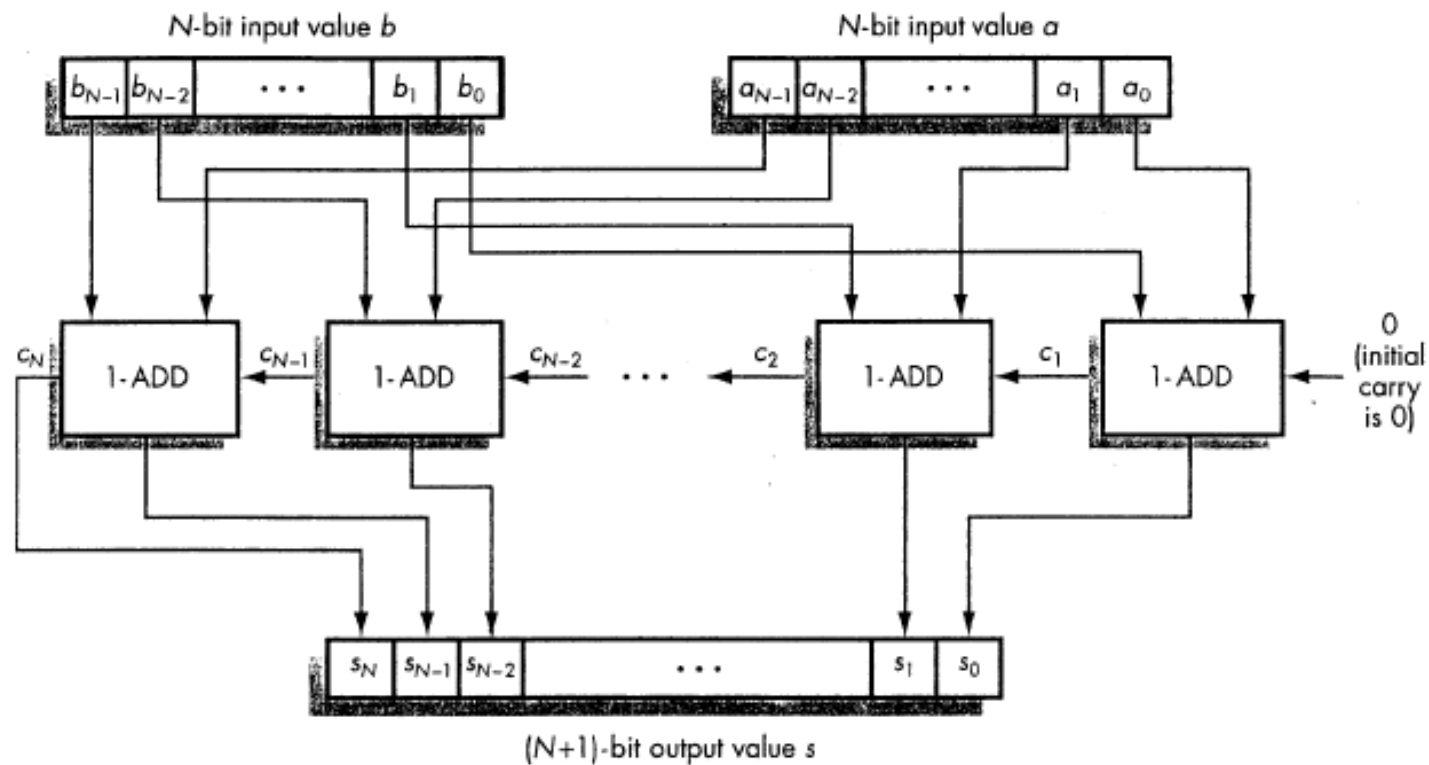

Timing Diagram


NOT gate

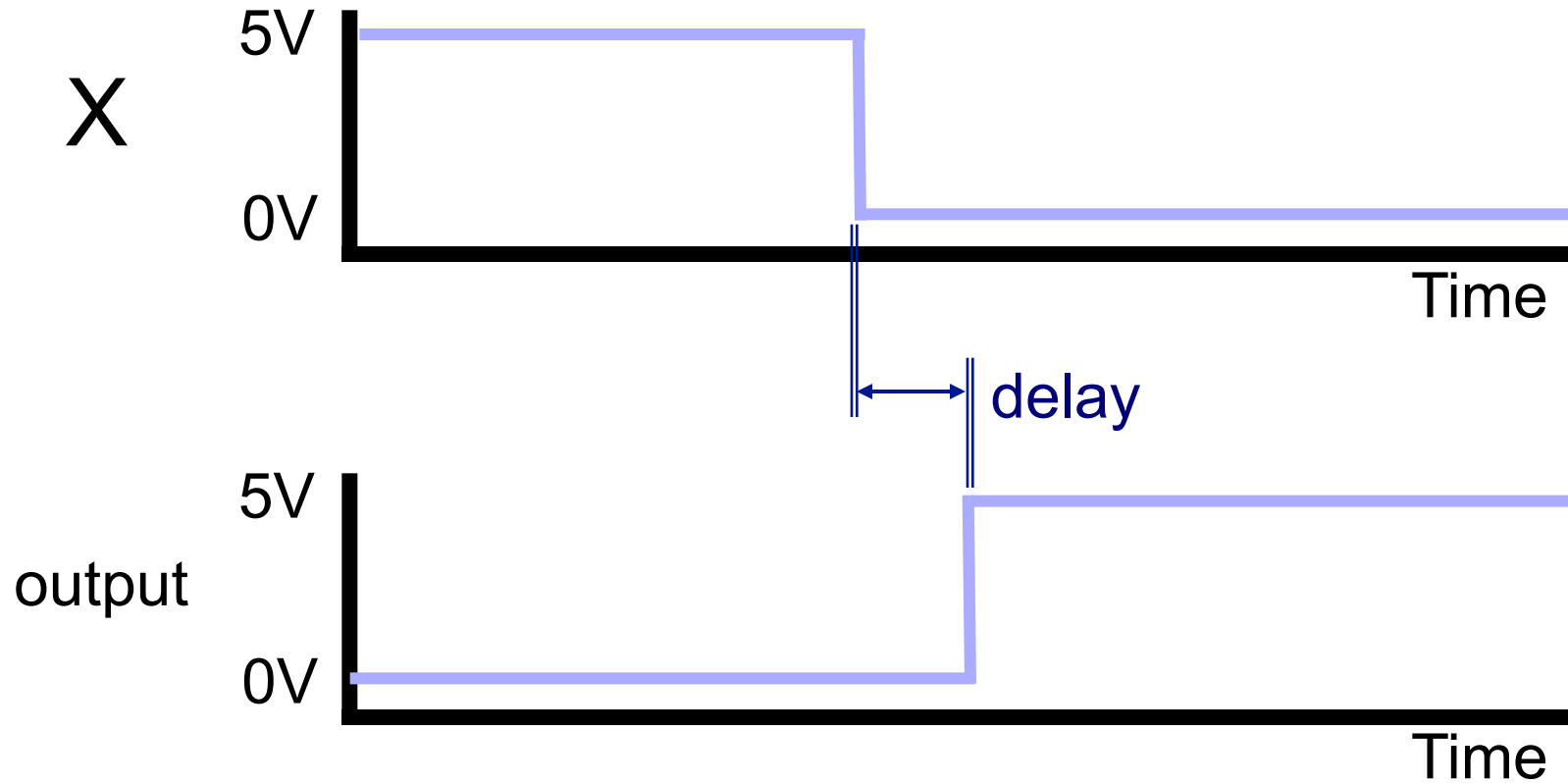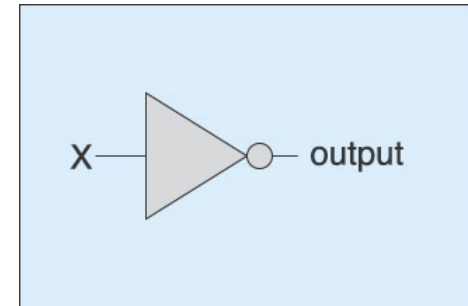



Memory

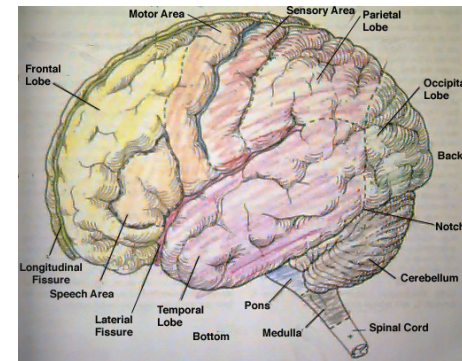Rest of this lecture:
How boolean circuits have “memory”.



What do you understand by ‘memory’?”?




How can you tell that a 1-year old child has it?

Behaviorist's answer:
His/her actions depend upon past events.




Why combinational circuits have no “memory”

- Boolean gates connected by wires

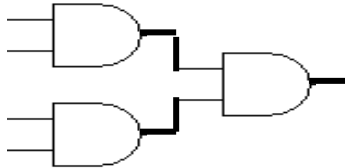

Wires: transmit voltage
(and hence value)

- Important: no loops allowed

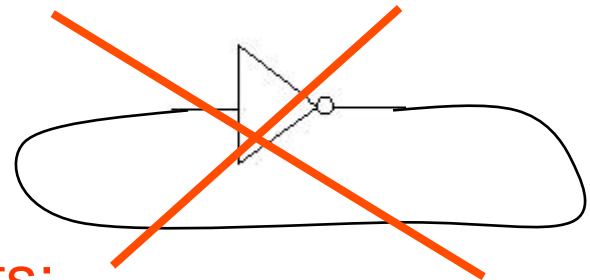


Output is determined by current inputs;
no “memory” of past values of the inputs.

Today: Circuits with loops; aka “Sequential Circuits”

Matt likes Sue but he doesn't like changing his mind

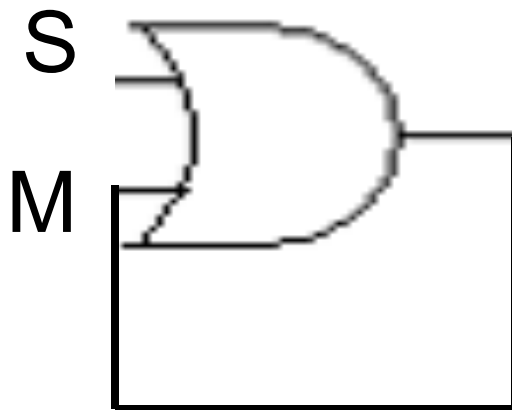- Represent with a circuit:
Matt will go to the party if Sue goes or if he already wanted to go



Is this well-defined?





Sequential Circuits

- Circuits with AND, OR and NOT gates.
- Cycles **are** allowed (ie outputs can feed back into inputs)
- Can exhibit “memory”.
- Sometimes may have “undefined” values

Enter Rita

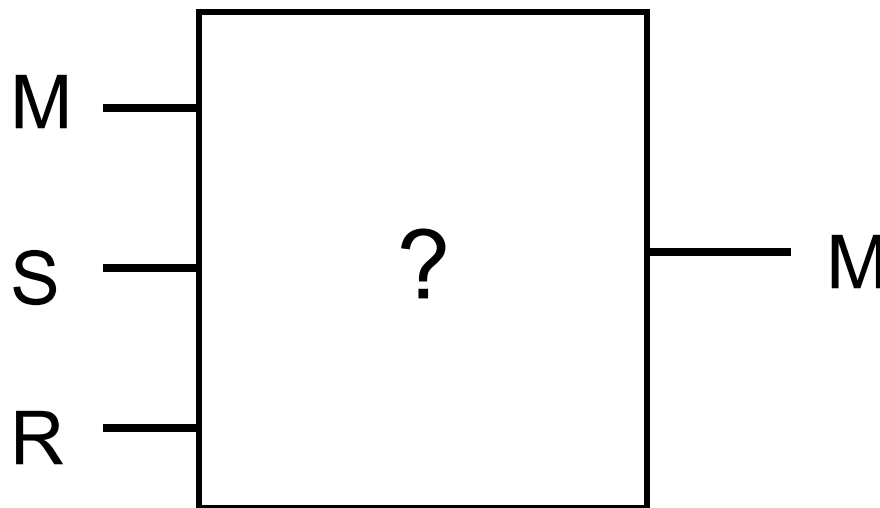
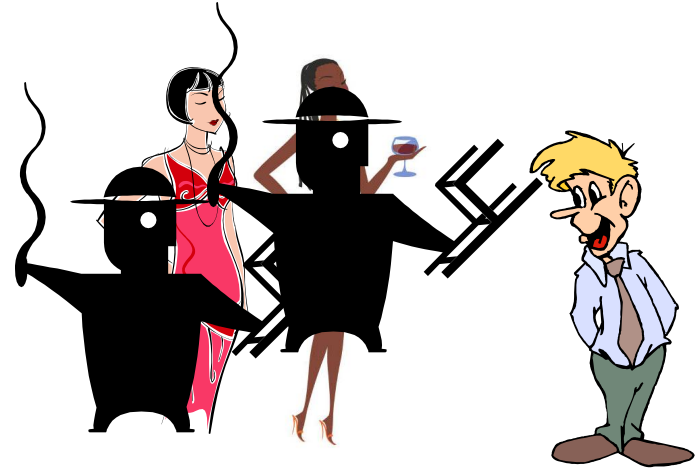
- Matt will go to the party if Sue goes OR if the following holds: if Rita does not go *and* he already wanted to go.



R, S: **“control”** inputs


What combination of R, S changes M?

R-S Flip-Flop

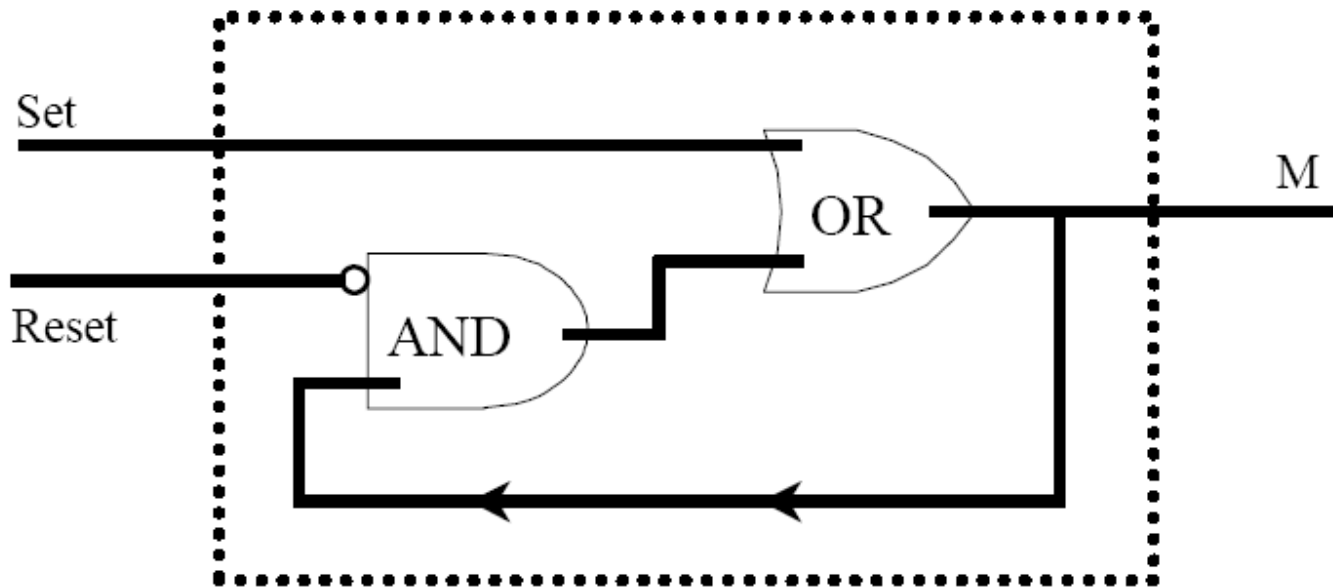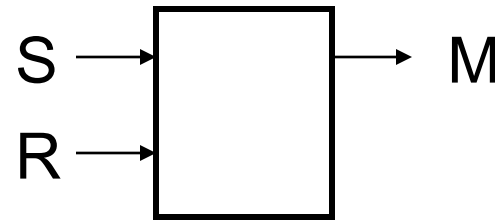

- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if both are 0), M just remembers its value

A more convenient form of memory

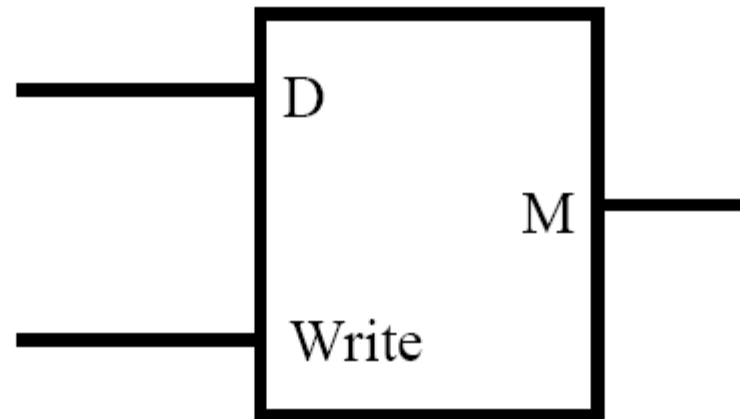


No
“undefined”
outputs ever!

- If $\text{Write} = 0$, M just keeps its value. (It ignores D .)
- If $\text{Write} = 1$, then M becomes set to D

Fact: “Data Flip-Flop” or “D flip flop”;
can be implemented using R-S flip flops.

“Register” with 4 bits of memory

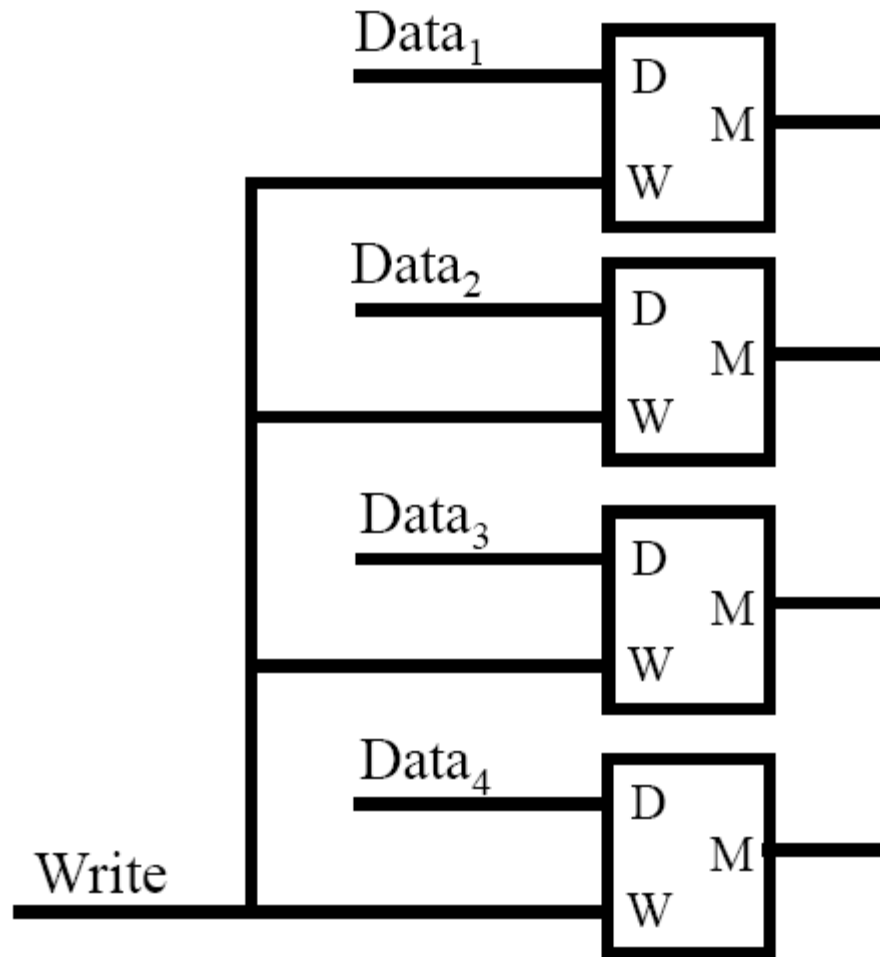


What controls the “Write” signal?

- Often, the system clock!
- “clock” = device that sends out a fluctuating voltage signal that looks like this




“Computer speed” often refers to the clock frequency (e.g. 2.4GHz)

The “symphony” inside a computer

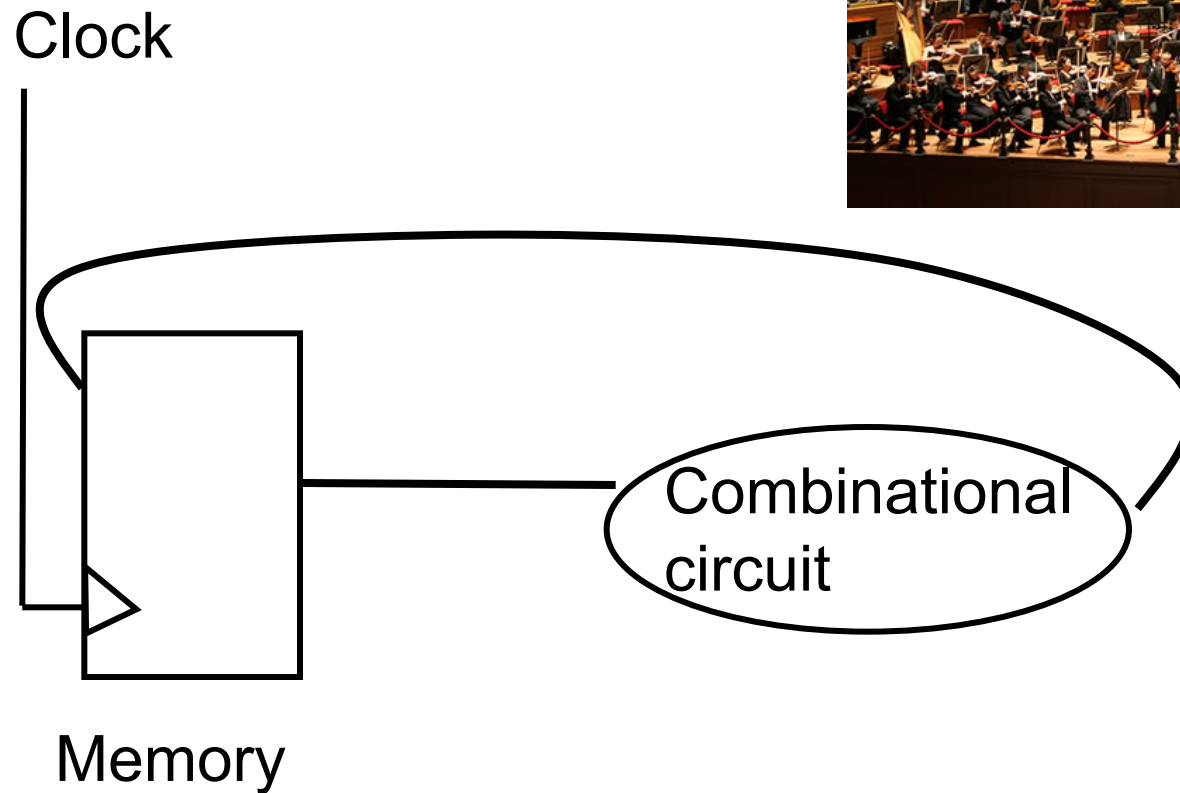

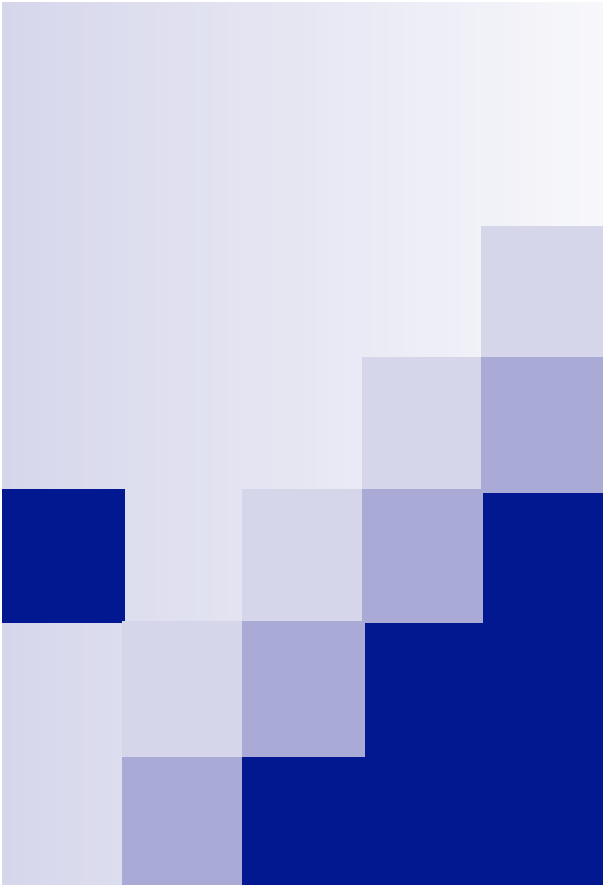
Clocked
Sequential
Circuit
(aka
Synchronous
Circuits)




Clocked Sequential Circuits

Synchronous Sequential Circuit

(aka Clocked Sequential Circuit)

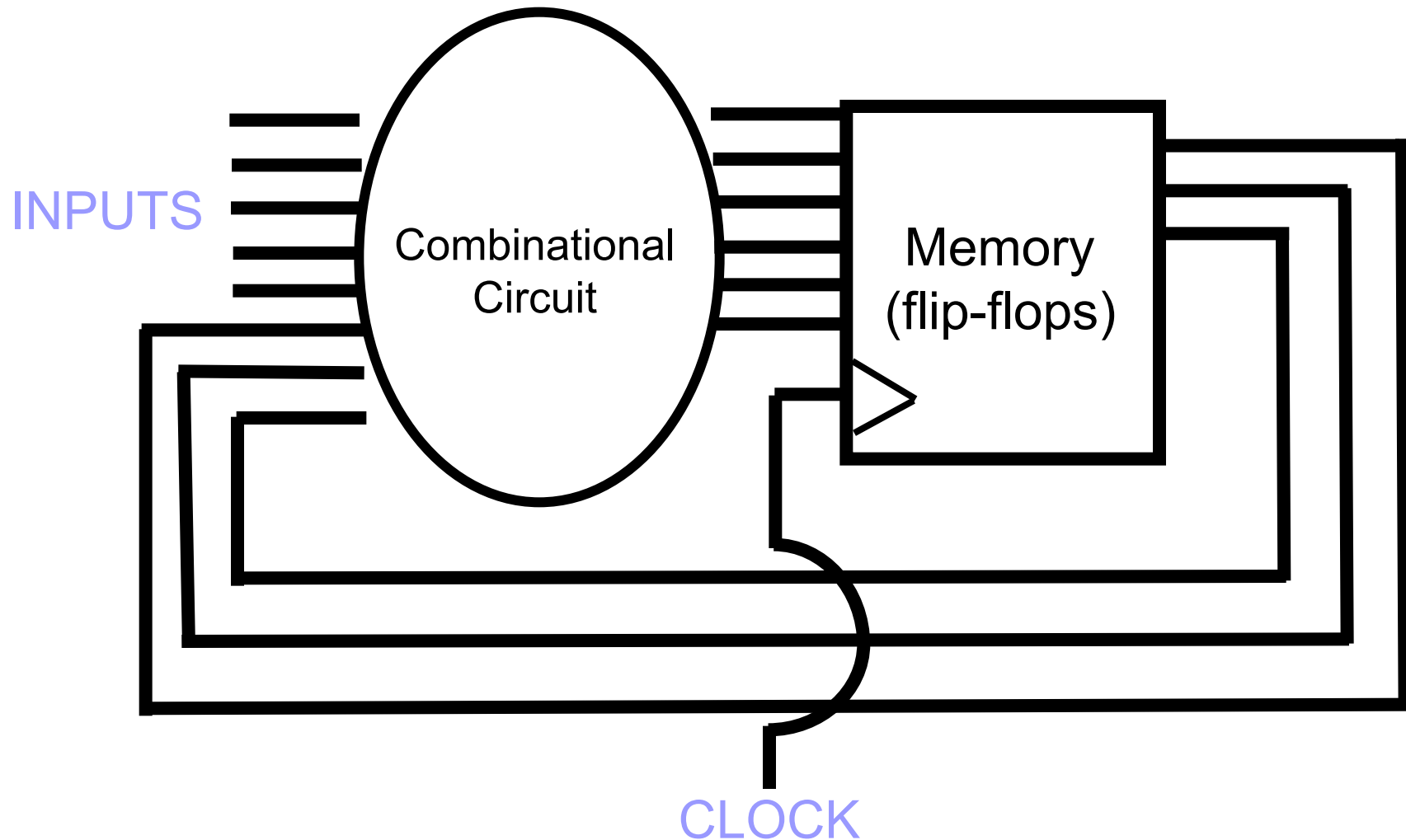


Shorthand

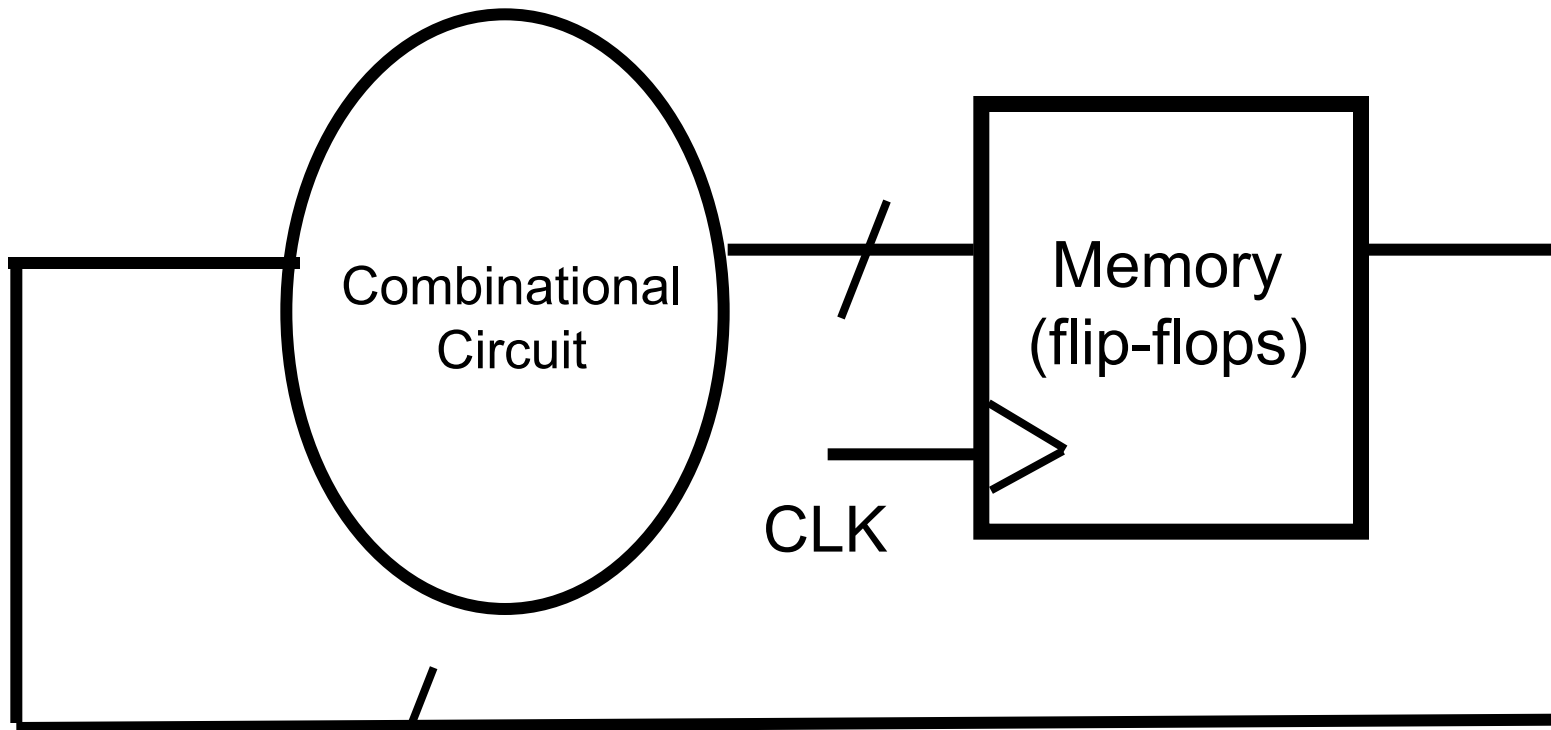

This stands for "lots of wires"


Clock Speeds

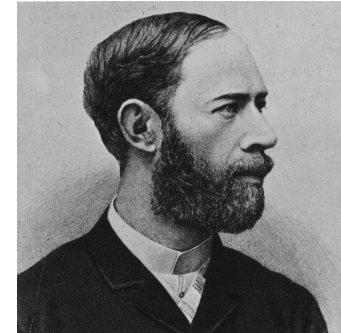

Heinrich Hertz
1857-94

| | | |
|------|-----------------|-----------------------------|
| 1974 | Intel 8080 | 2 MHz (Mega = Million) |
| 1981 | Original IBM PC | 4.77 MHz |
| 1993 | Intel Pentium | 66 MHz |
| 2005 | Pentium 4 | 3.4 GHz (Giga = Billion) |

What limits clock speed?

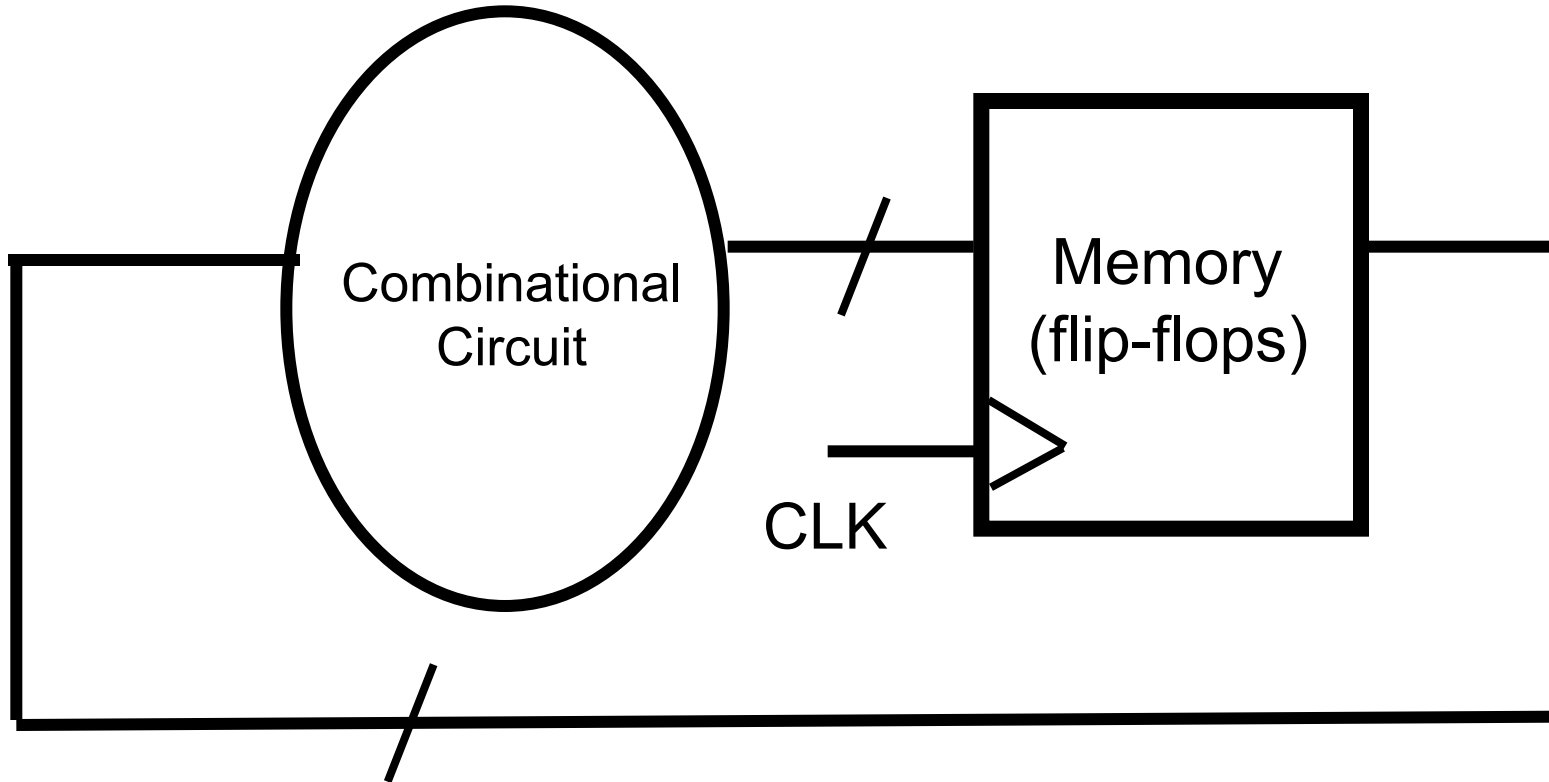

Delays in combinational logic (remember the adder)

During 1 clock cycle of Pentium 4, light travels: **4 inches**



Next two lectures...

- Computer organization: CPUs and RAM
- Lessons from computer architecture.

- Guest lecturer: Szymon Rusinkiewicz